

科环2012



# 电磁兼容原理与应用整改 EMC & its Design

报告人：和军平（Dr.）

Apr,6, 2012  
Shenzhen City  
[hejunping@hitsz.edu.cn](mailto:hejunping@hitsz.edu.cn)

## 内 容


- 一. 开关电源干扰形成机理
- 二. 无源EMI滤波器设计
- 三. 新型EMI抑制技术
- 四. 滤波器的特殊问题

# 一：电力电子装置的传导电磁干扰发射(150kHz–30MHz)

## 1. 1 电力电子装置传导干扰发射基本原理


### 1. 1. 1：测试布局和检测量

单相：L, N line

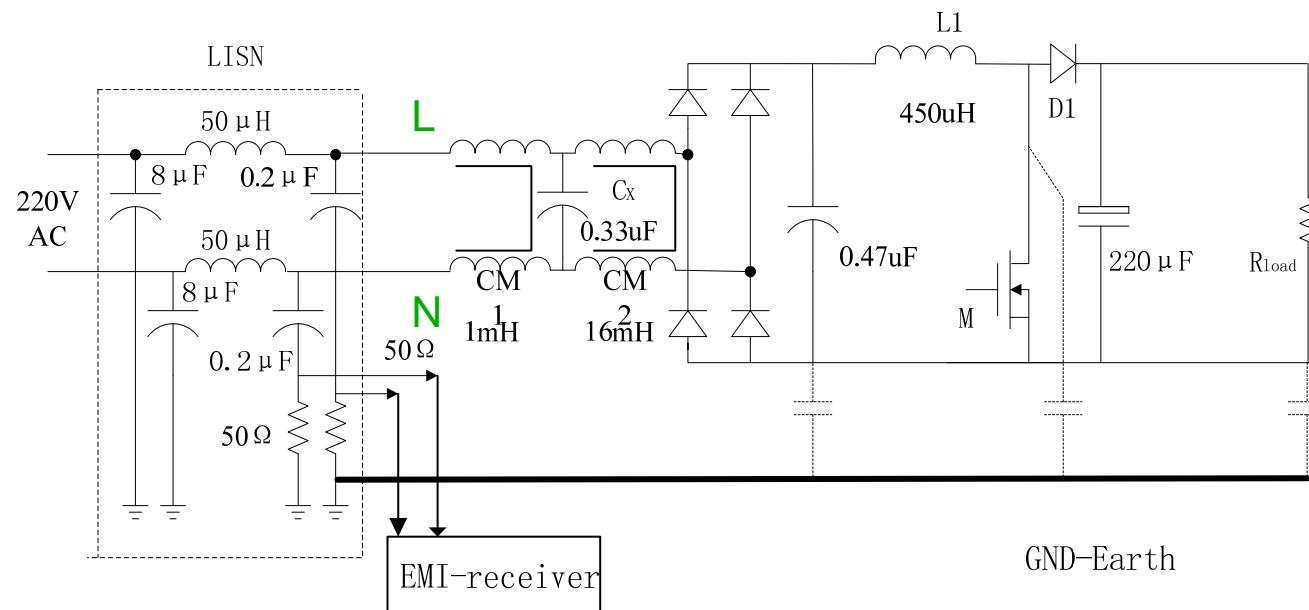

EMI接收机测量上述线上的射频干扰量值，均要小于限值

三相: L1, L2, L3, Earth

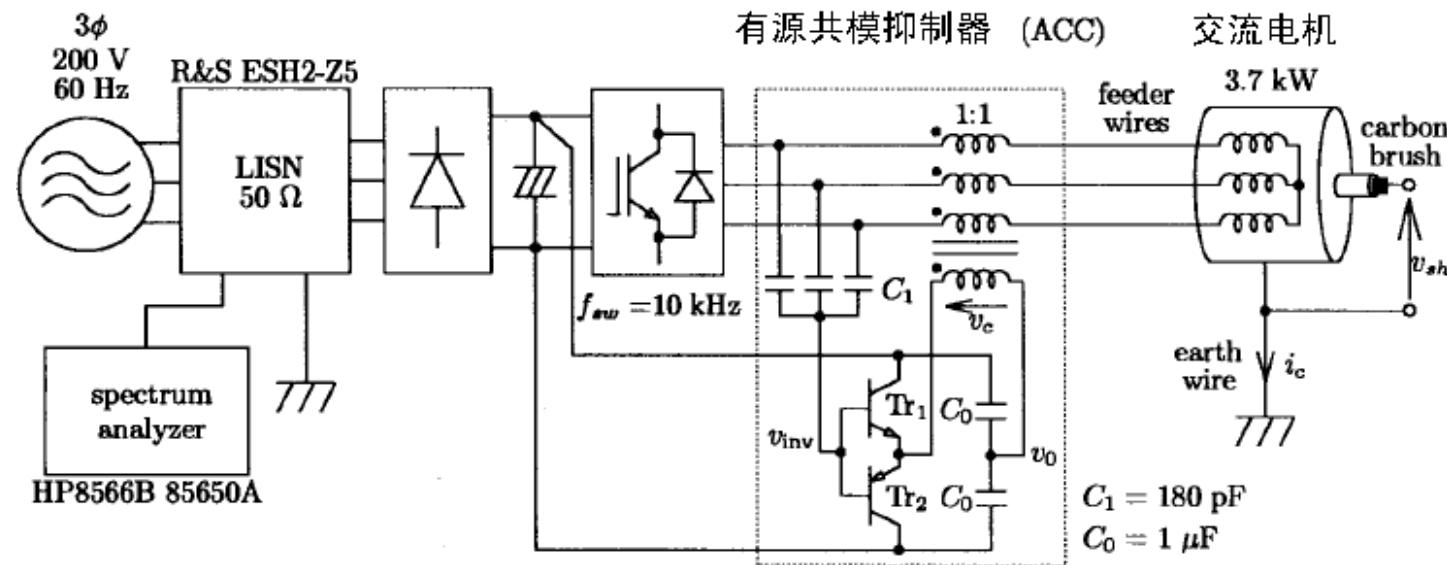


EMI接收机测量上述线上的射频干扰量值，均要小于限值

## 1.1.2 电力电子装置电磁干扰的产生源头和传播机理

*Three factors of EMI!    EMI source, coupling paths, sensitive objective*

电磁干扰产生的源头

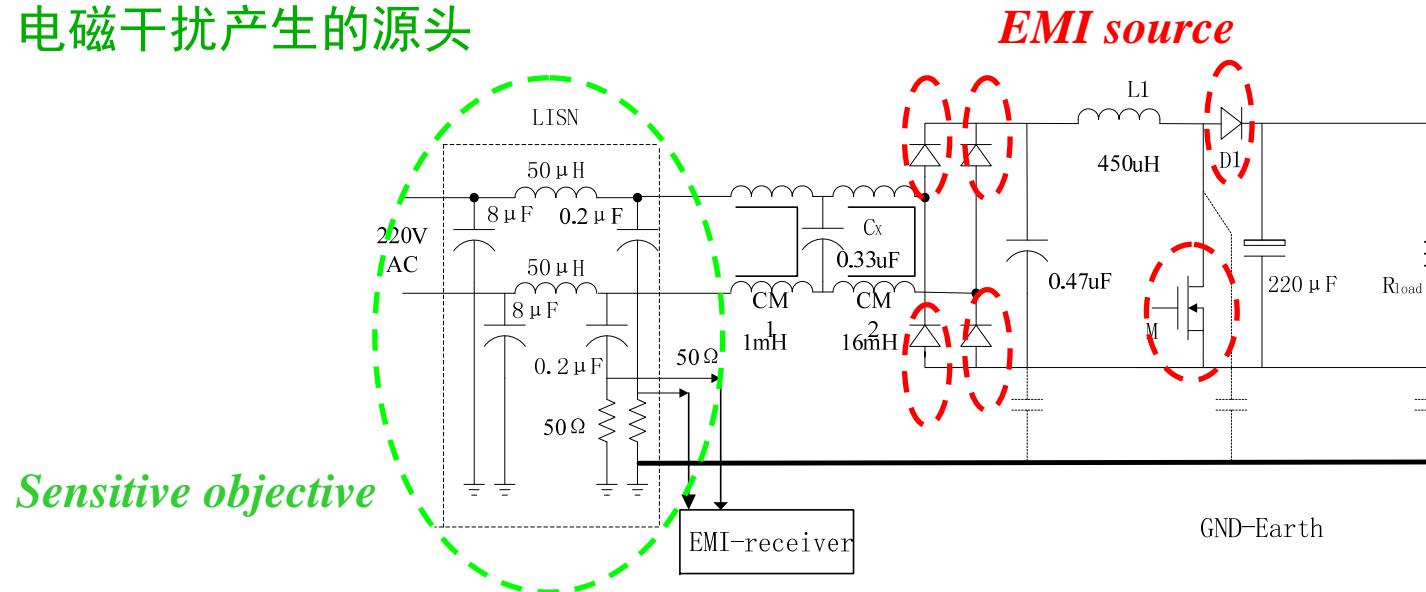

*There are lots of different opinions. Mosfet, Diode, transformer, AC loop etc*



*Strictly speaking,*


**Only Nonlinear switching devices are true EMI sources for EMI emission!**

**Others are coupling paths!**

*Only for Radiation emission or simply analysis, others transformer and AC loop can be treated as EMI source!*

### A: Diode turn-on and turn-off

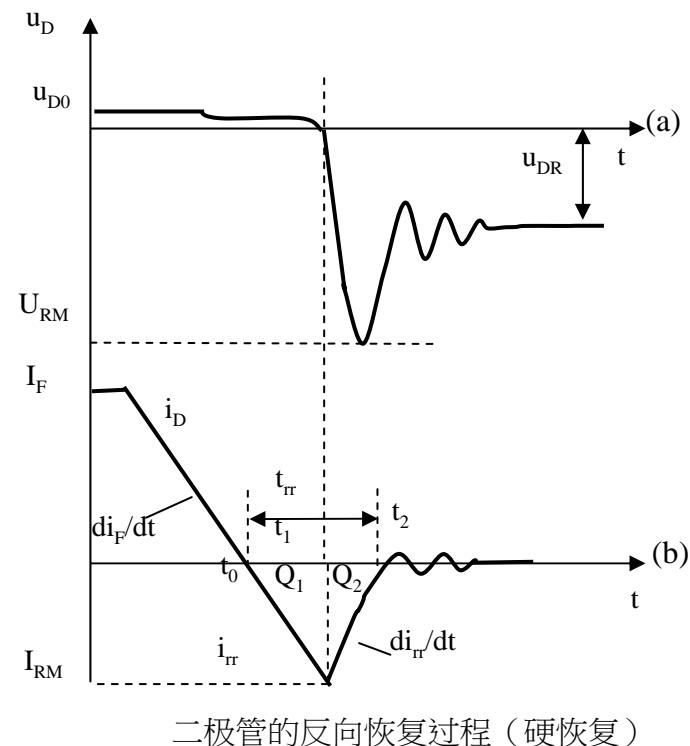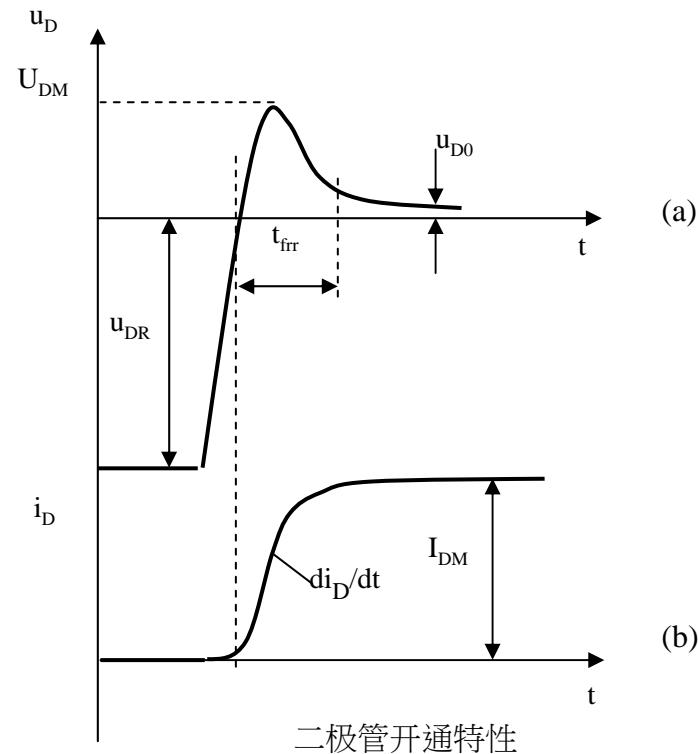


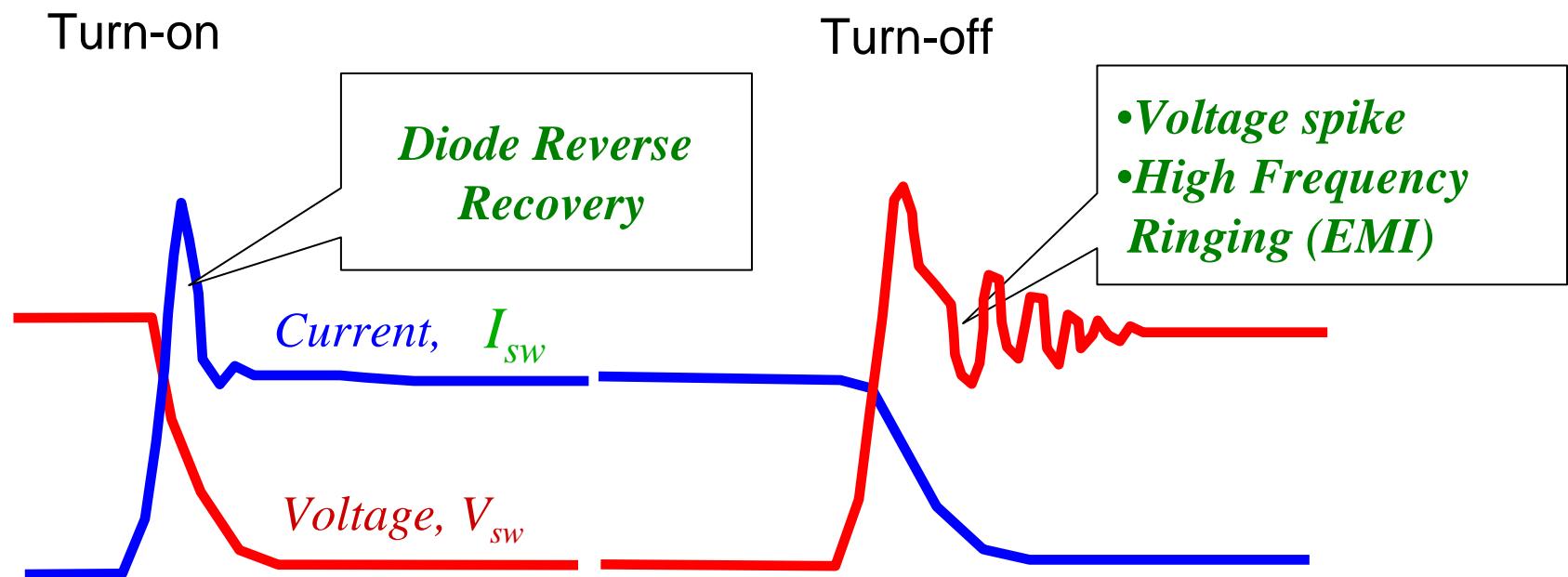**B:** Transistor turn-on and turn-off

*How about coupling paths! The difficult factors!*

*Basic EMI coupling mechanism*

A: *Along metal Lead*

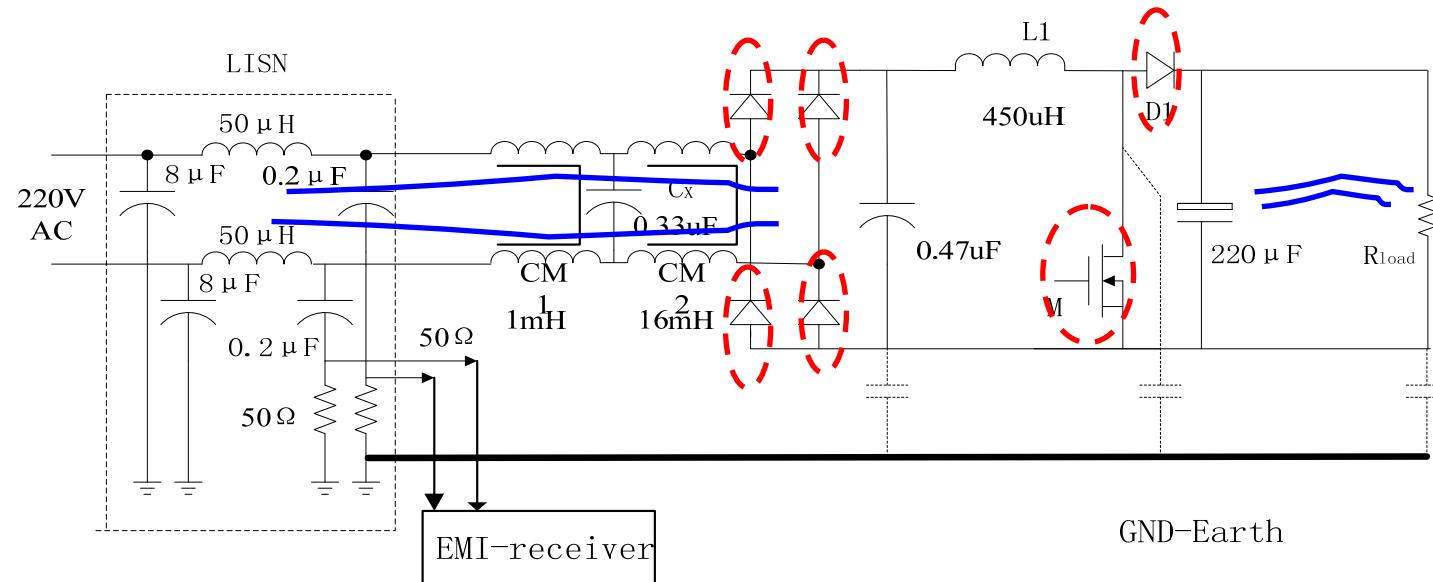


## Basic EMI coupling mechanism

B: space Induct effect

B1: Capacitive coupling effect:


***There is a coupling capacitor between every-two conductors!***

Trace

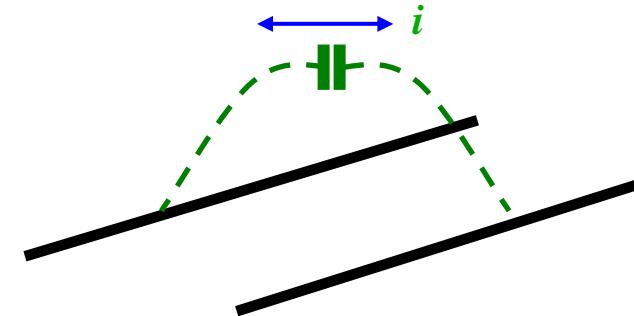



$$C_{12} = k \frac{S_1 S_2}{D}$$

Transformer


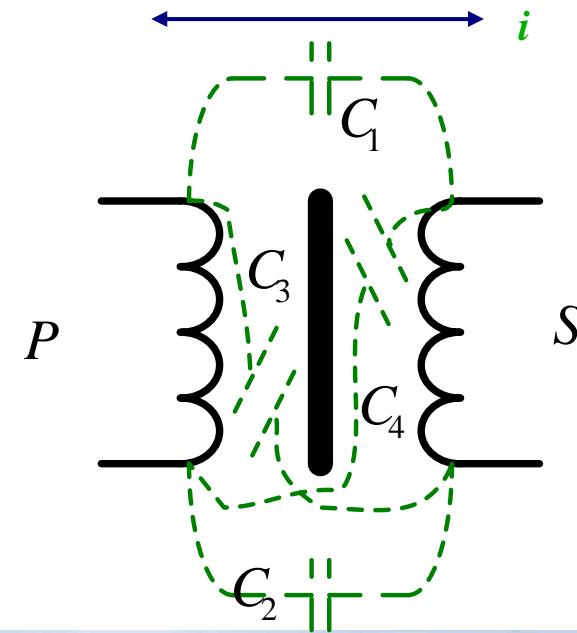


B1: Capacitive coupling effect:

*Capacitor between drain to heatsink*

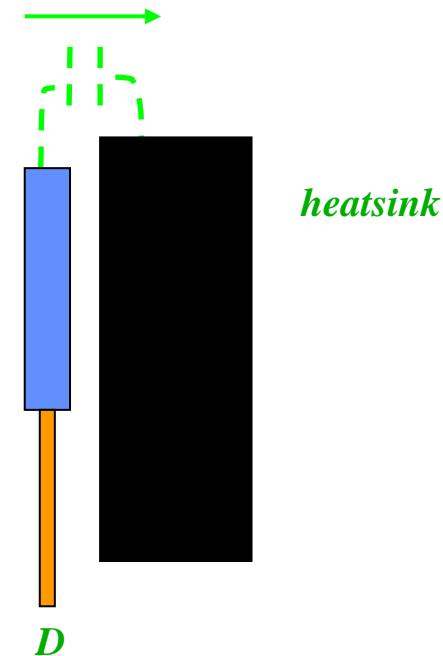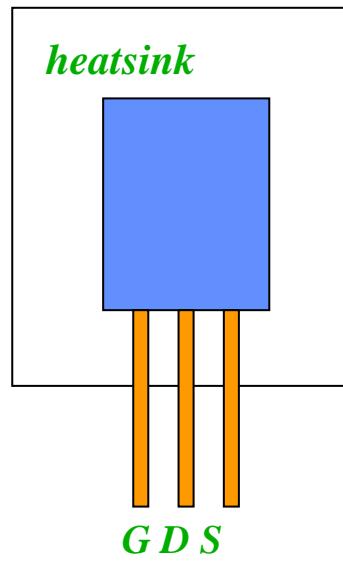

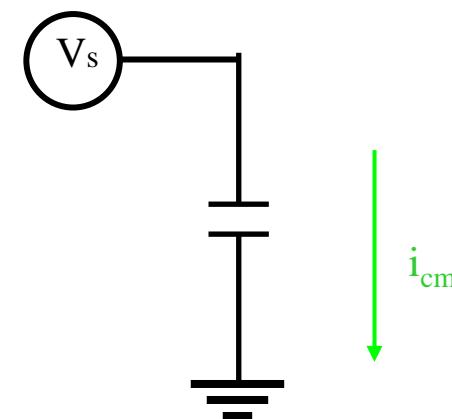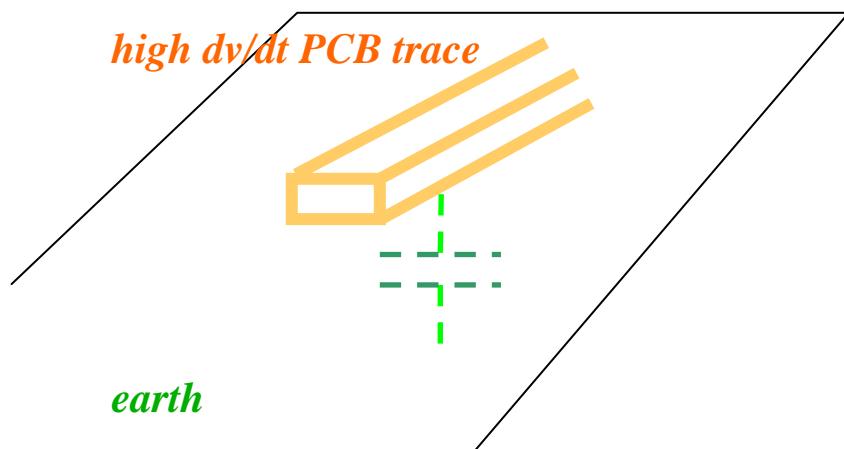*Capacitor between high dv/dt trace or metal to earth*





B2: Inductive coupling effect:



**There is a coupling inductor between every-two loops!**

Typical magnetic loops:




**Inductor1: Transformer:**

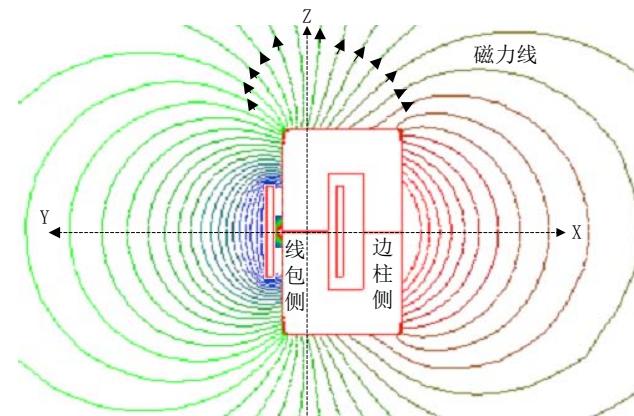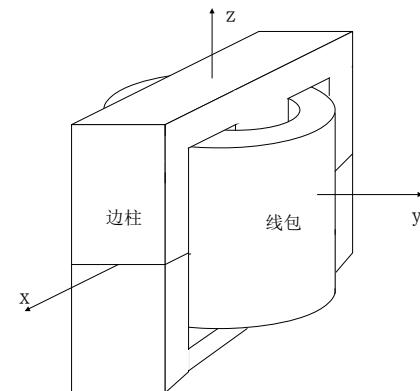

**Inductor2:**

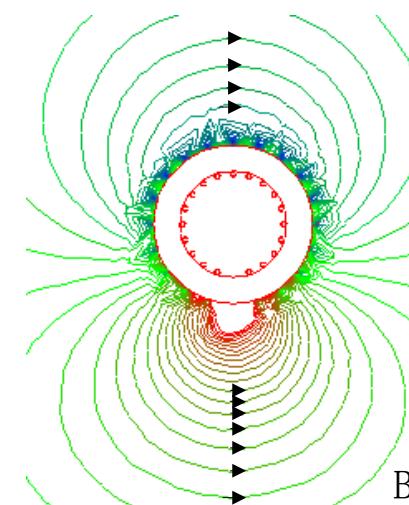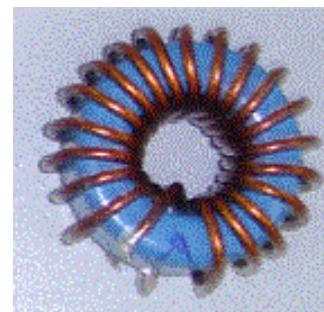

## High frequency AC loops

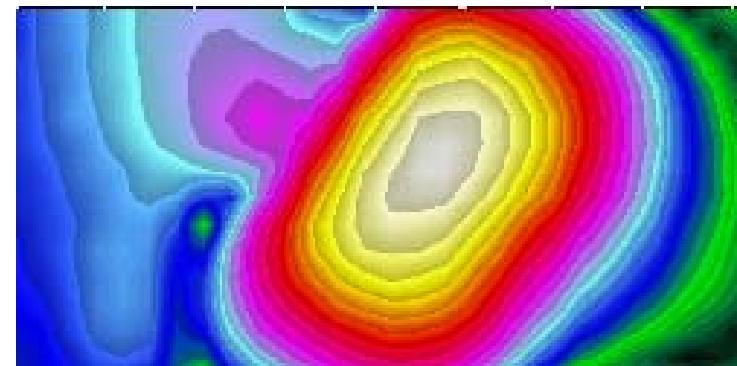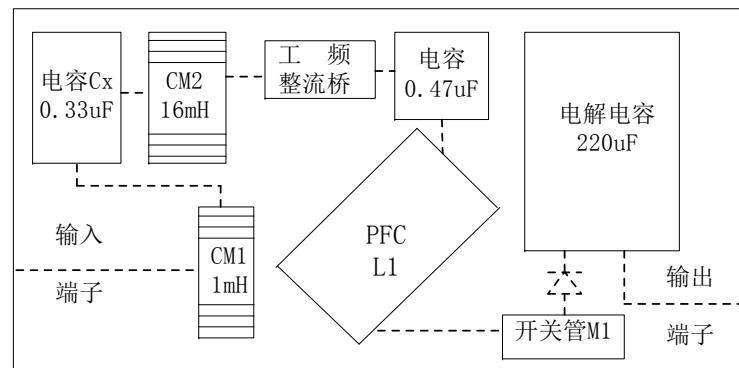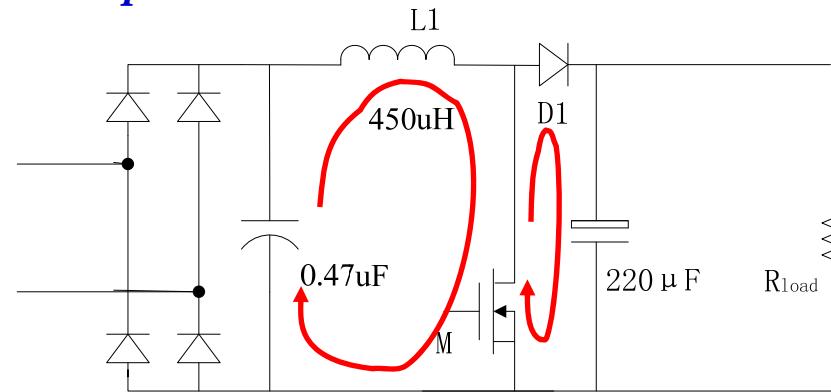


*Inductive coupling: produce EMI directly some time → sensitive circuit  
complicit EMI coupling paths. → influence EMI filter performance.*

### 1.1.3 电力电子装置电磁干扰的共模/差模分析

*Why?*

**Example: Single phase**

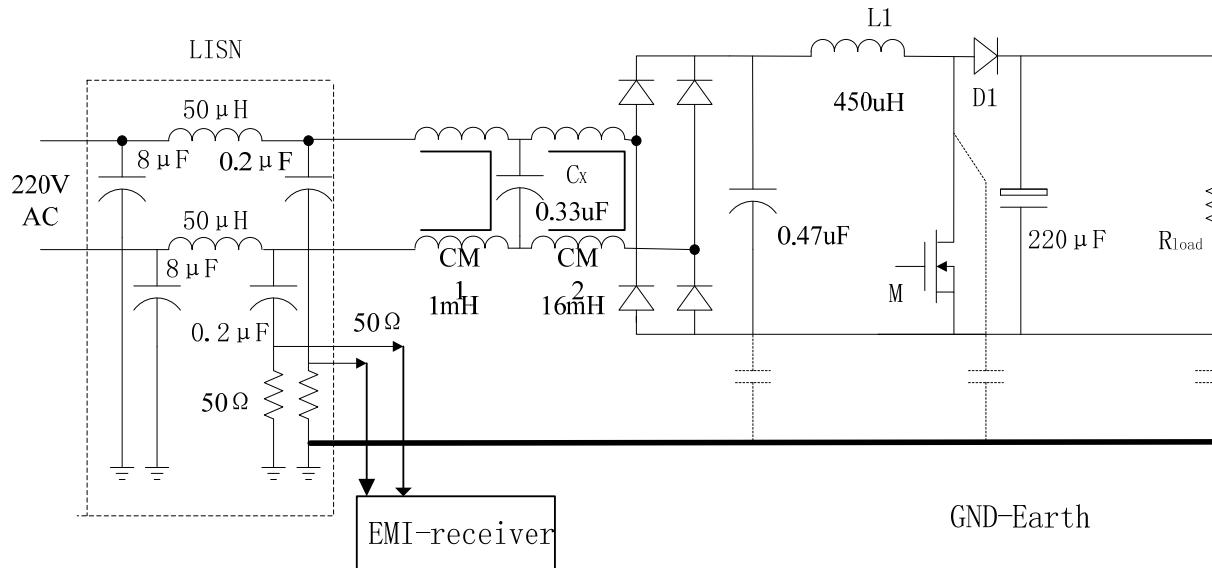

Emission on L line:  $V_L$

Emission on N line:  $V_N$

$$V_{CM} = (V_L + V_N) / 2$$

$$V_{DM} = (V_L - V_N)$$

$V_{cm}$  &  $V_{dm}$

$$V_L = V_{CM} + V_{DM} / 2$$

$$V_N = V_{CM} - V_{DM} / 2$$

So,  $V_L$  &  $V_N$     $V_{cm}$  &  $V_{dm}$  are same!

**Why?** 因为差模回路和共模回路有不同的特点和性质，分开考虑，  
便于把握EMI形成、传播和抑制。

差模回路： voltage or current between L&N or among L1、L2、L3

*Equivalent internal impedance is small! Paths is clear!*


*Through lines-load*

共模回路： voltage or current between lines and Earth


*Equivalent internal impedance is large! Paths is unclear in most case!*

*Through parasitic capacitor*


Example1 of Flyback

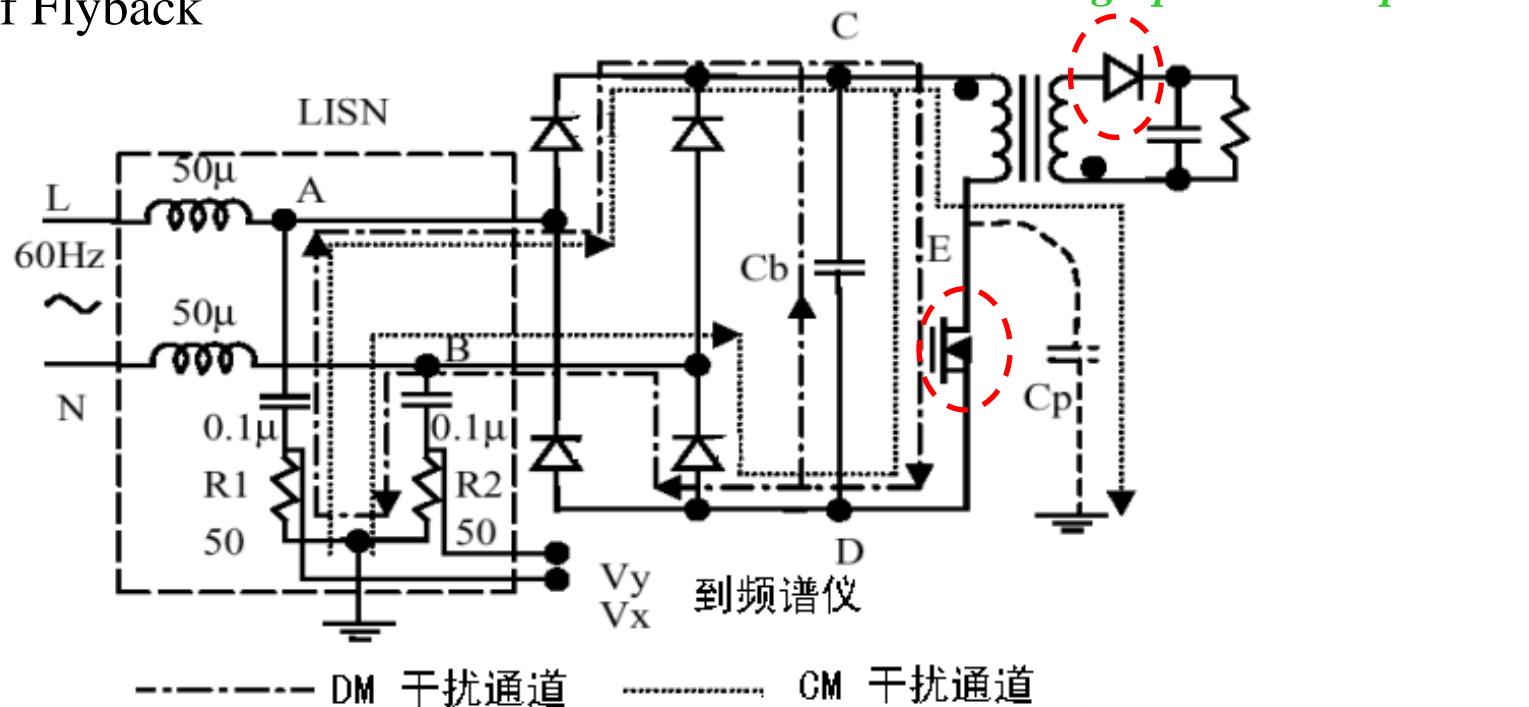

## Example2 of a Boost PFC

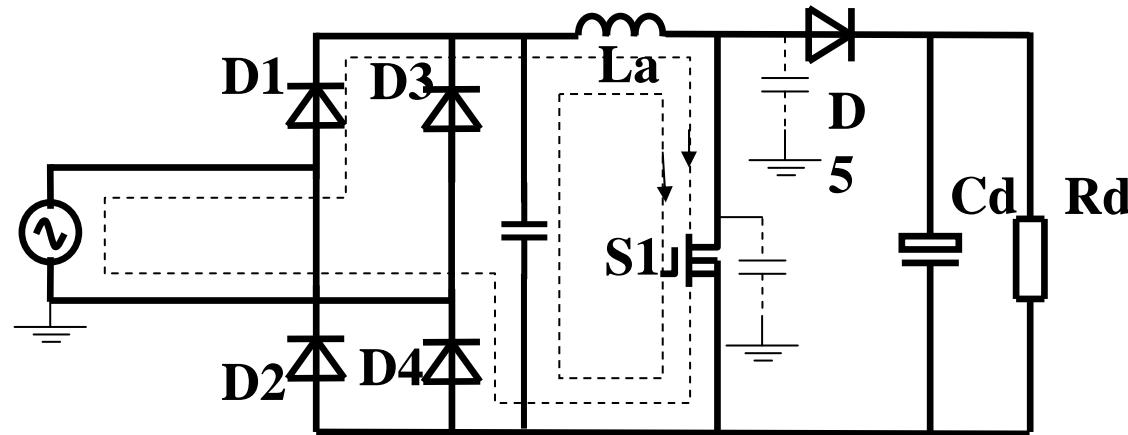


Noise Path of DM Noise without LISN

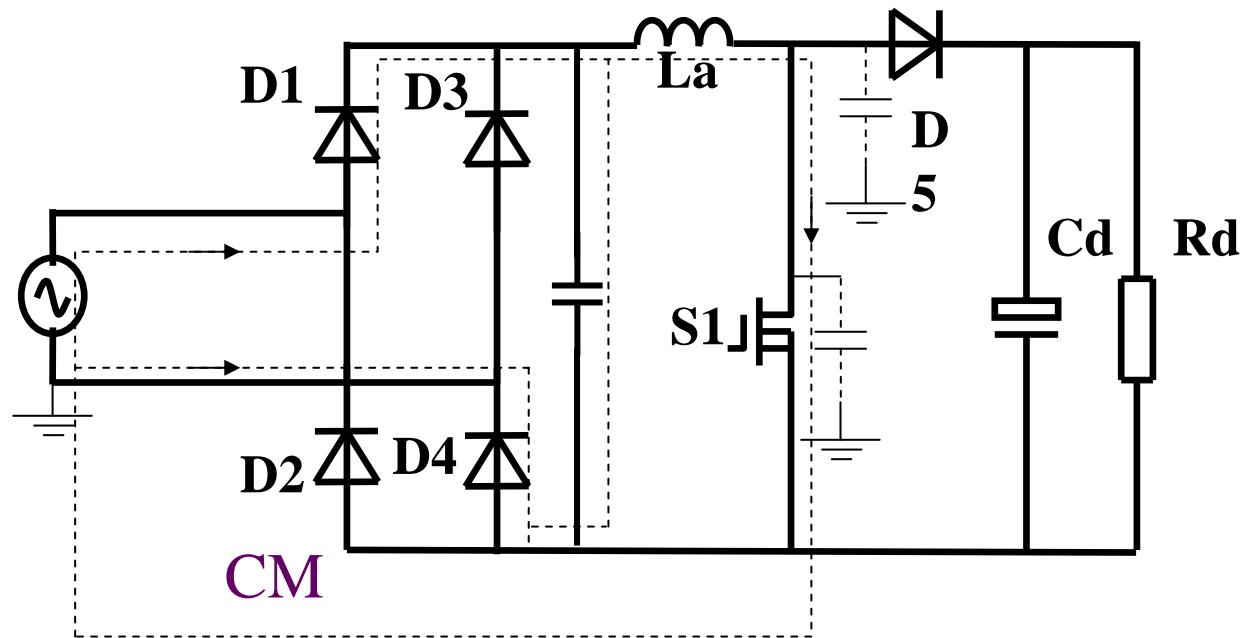

Noise Path of CM Noise without LISN


### Example3 of a INVERTER

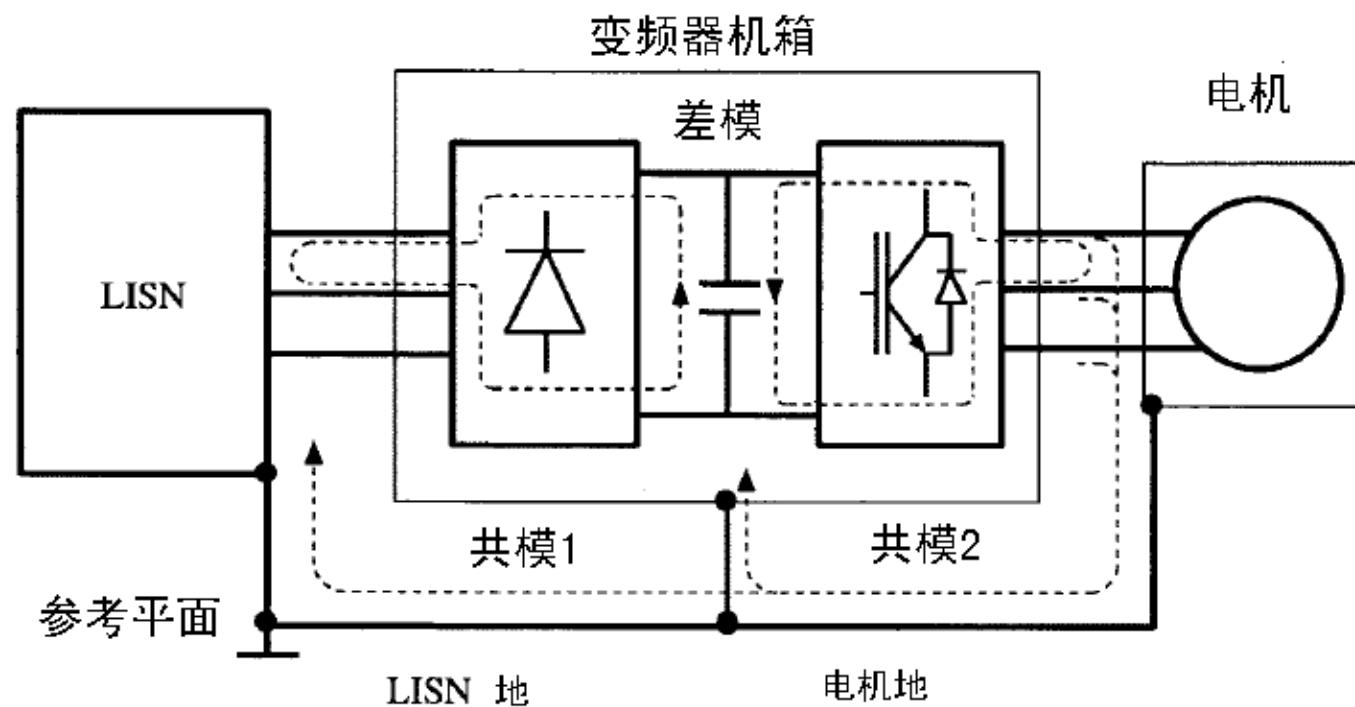
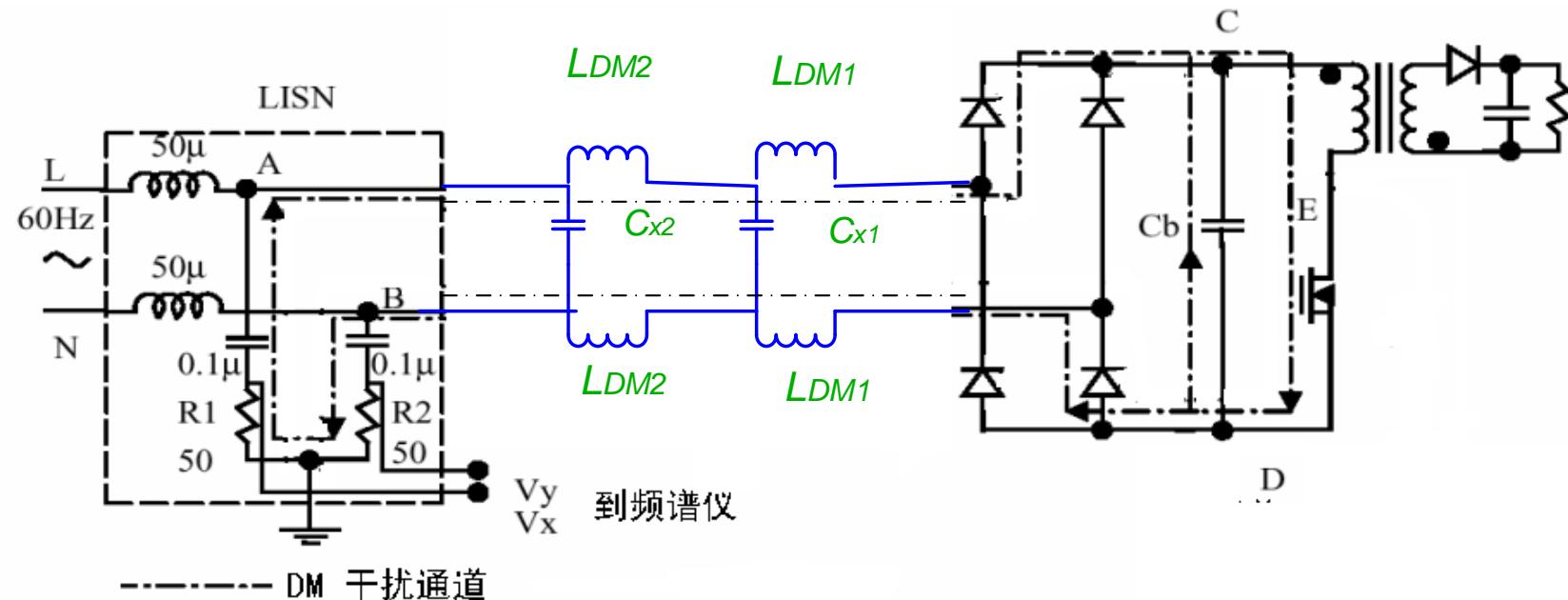
## Usefulness of DM/CM Analysis:


*It is very useful for EMI filter design and EMI debug!*

*DM EMI filter to control DM emission! It has no influence on CM EMI.*




*Generally, Cx is large several uF, Ldm is small!*

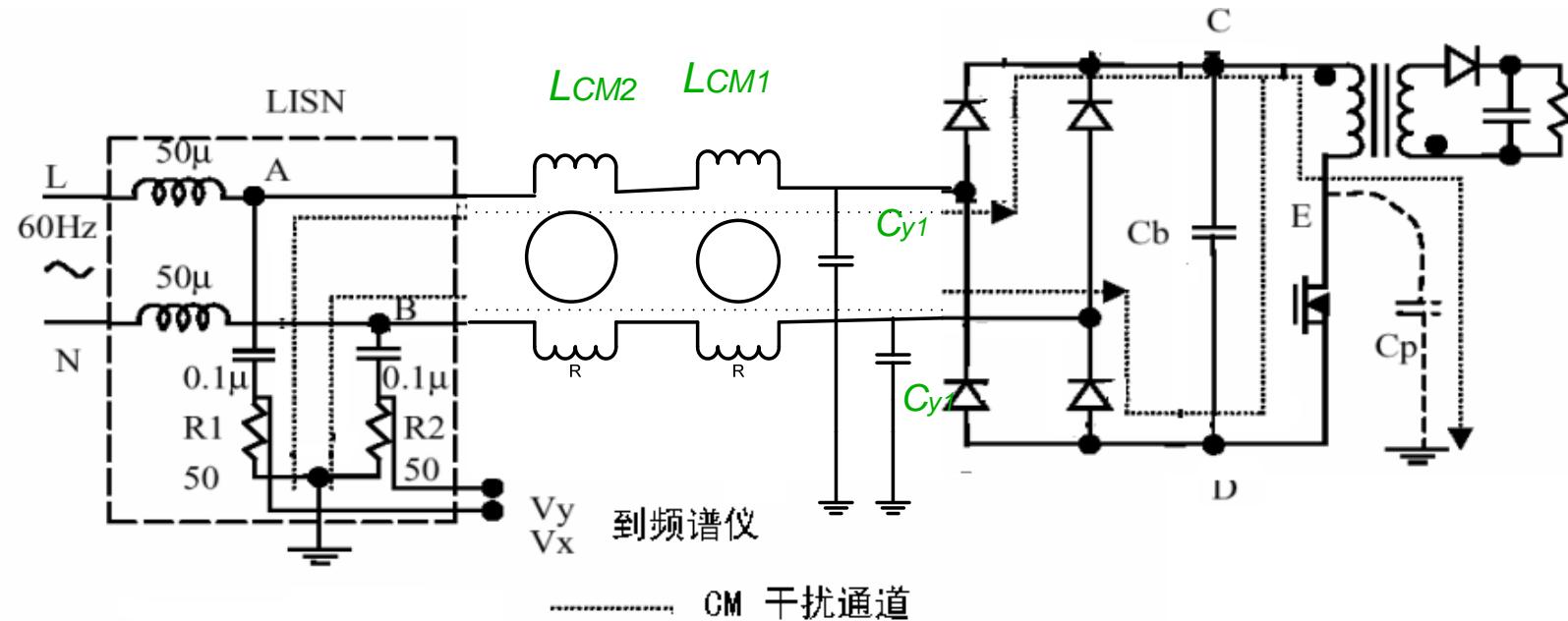CM EMI filter to control CM emission! It has no influence on DM EMI.



An actual EMI filter to control EMI emission!

CM filter+DM filter

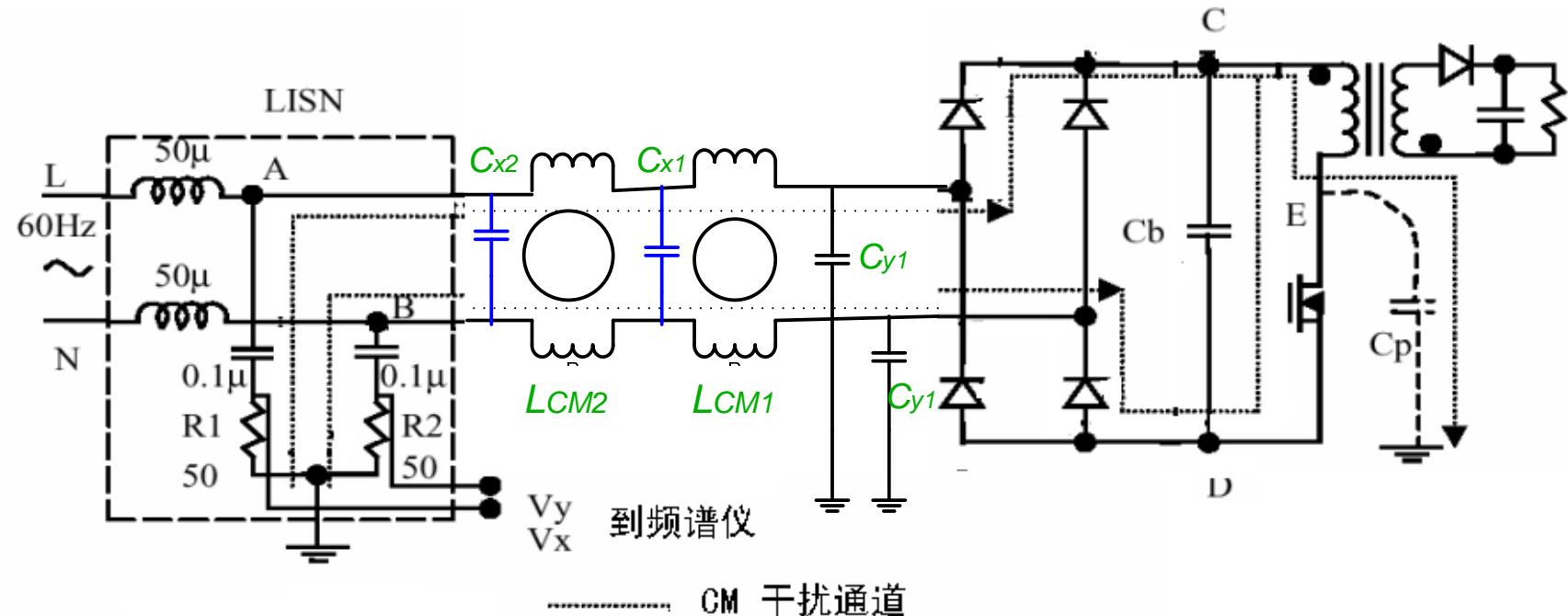


The leakage inductance of CM choke can be used as LDM

## 二 电力电子装置EMI滤波器抑制技术


### 2. 1 EMI滤波器的设计和使用

Insertion Loss Definition

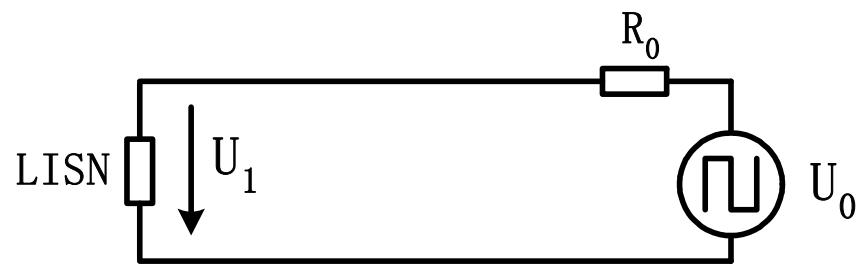

$U_0$ : Noise Source

$R_0$ : Noise Source Impedance

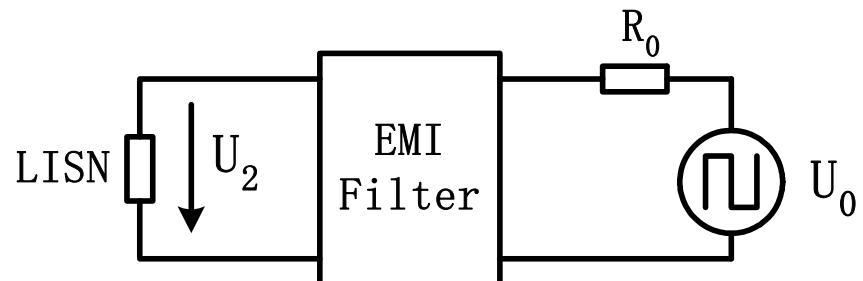


$U_1$ : Voltage on LISN when  
without Filter

$U_2$ : Voltage on LISN when  
with Filter

$$IL = 20 \log\left(\frac{U_1}{U_2}\right)$$
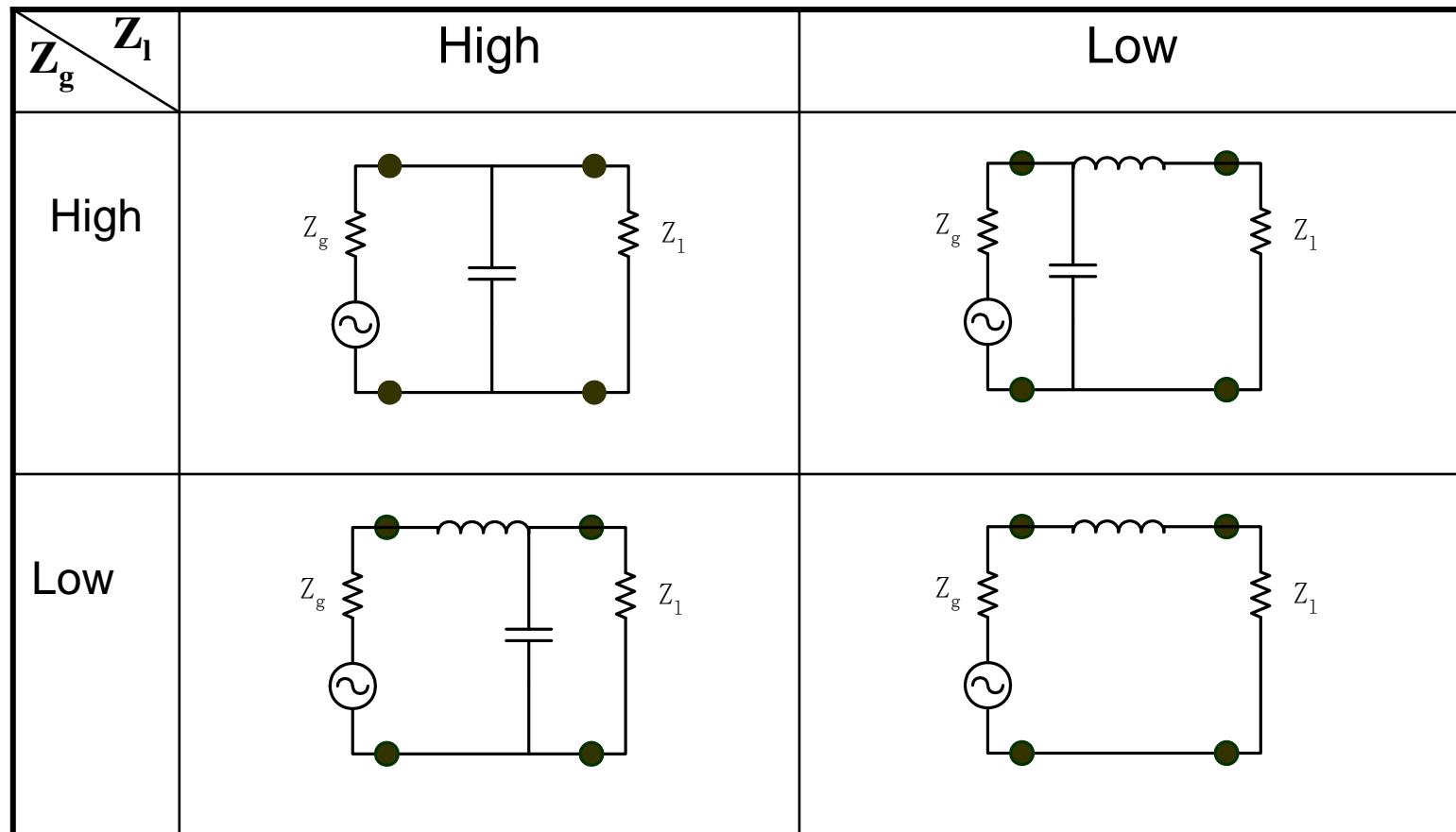
## A: How to select the best EMI filter topology?




$Z_g$ : Noise Impedance


$Z_l$ : LISN Impedance

If one stage is not enough, several stages filter can be used!

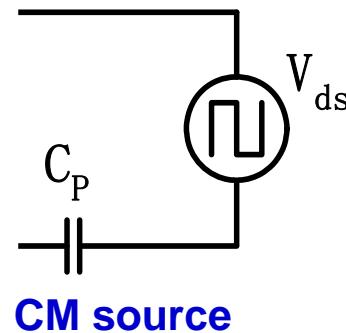Power supply EMI can be separated into equivalent CM/DM EMI source model.




CM source

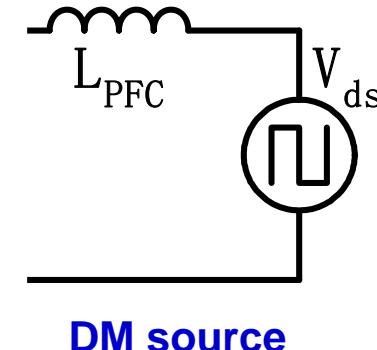

DM source

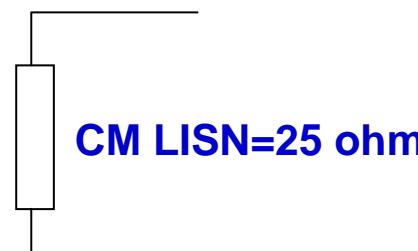Generally—internal DM source impedance is small!  
internal CM source impedance are large!




CM LISN=25 ohm




DM LISN=100 ohm

Generally—Both LISN DM impedance and CM impedance are small!

## So, better CM filter topology


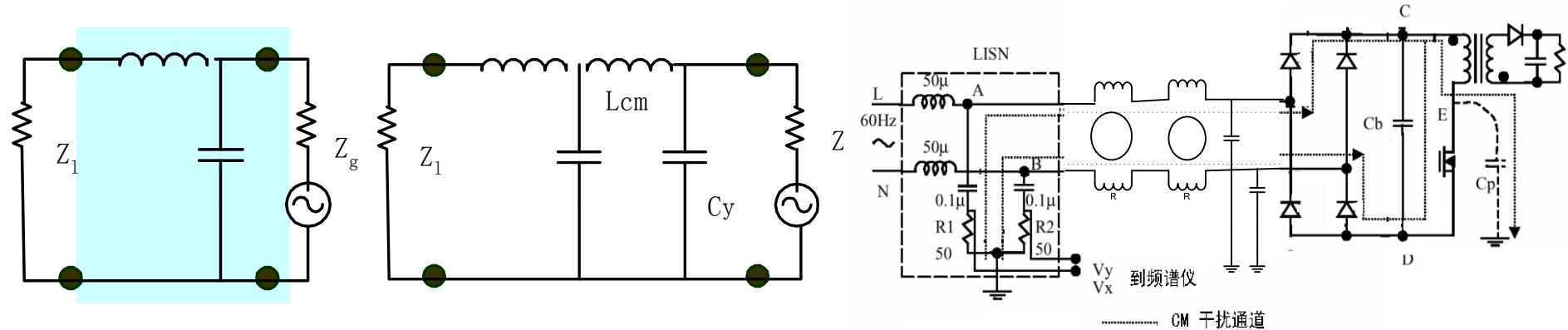


## So, better DM filter topology

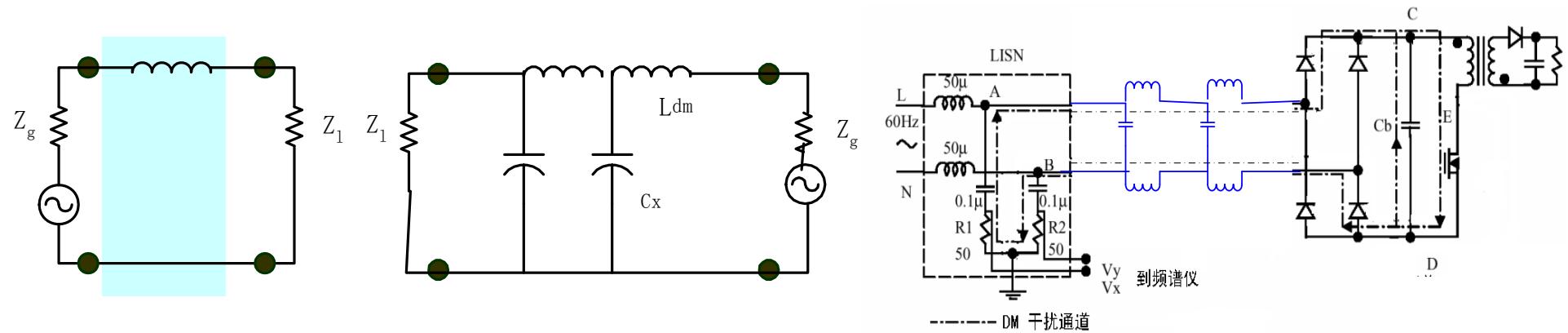

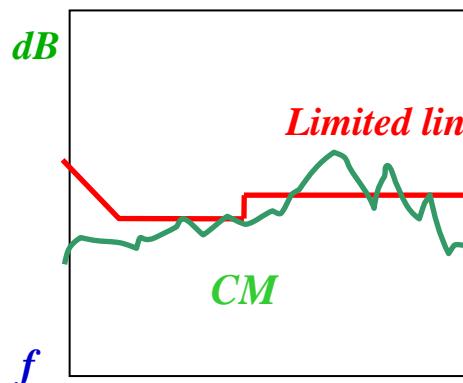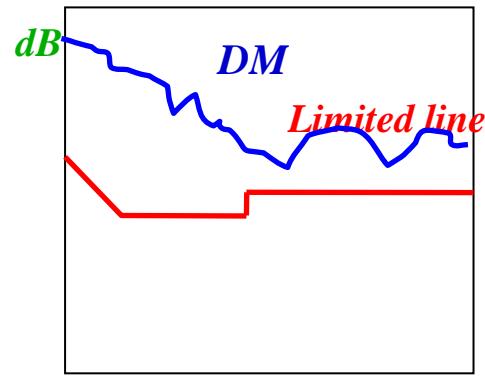
## B: How to decide inductance, capacitance value of EMI filter topology?


**Step1:** Separate CM/DM emission using test or simulation results!



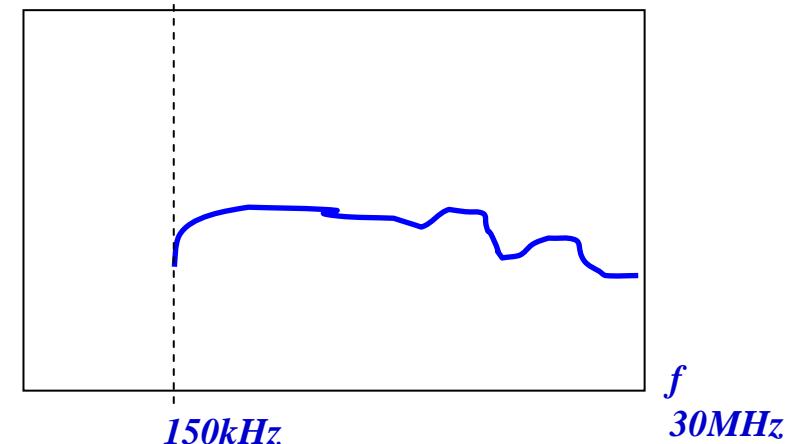
**Step2:** Using CM/DM emission decrease limited line, the IL needed of filter are gotten.



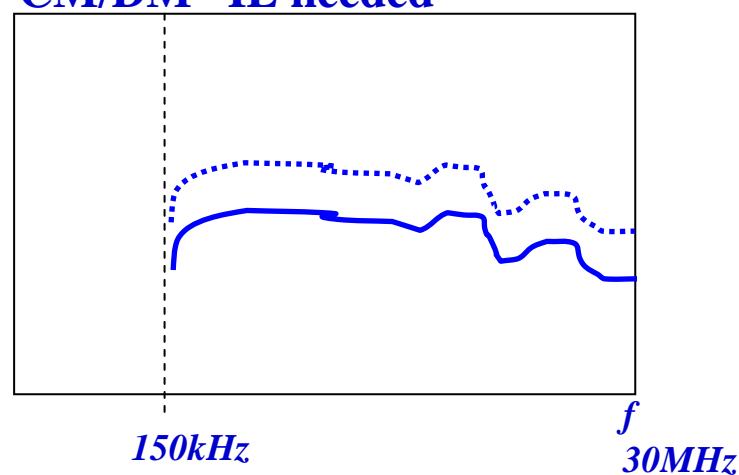**Step3:** adding 10 dB margin for both CM/DM IL needed



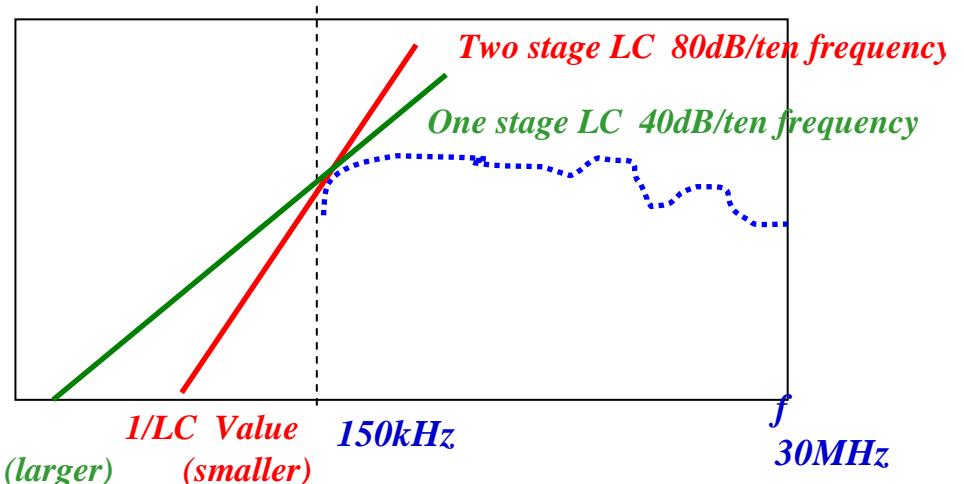
**Step4:** According LC number, draw N\*40dB line which is tangential to dot IL line.




**Step5: LC value, consider other factor, we can decide L and C.**

For CM, the max Cy value is limited by leakage current, so  
 $L_{cm}=f_0/C_y$ .

Lcm is called CM choke too.

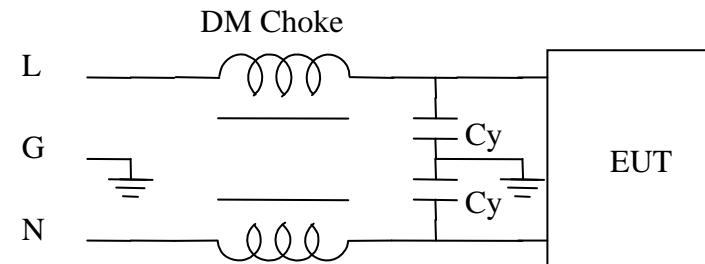


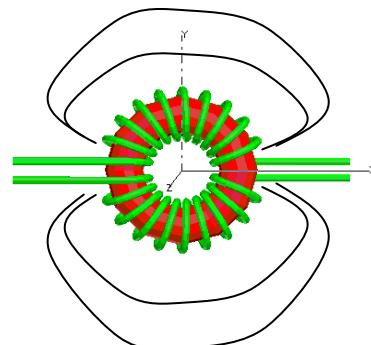For DM, for  $C_x$  can be easy large enough,  $L_{dm}$  is select small. In most case  $L_{dm}$  can be replaced by the leakage inductor od CM choke.






*leakage inductor*

**Step6: finish design and test.**

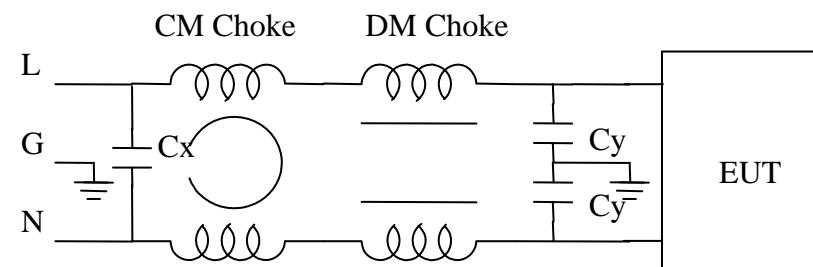


C: Actual problem during EMI filter use

1: HF IL are lower than expected.

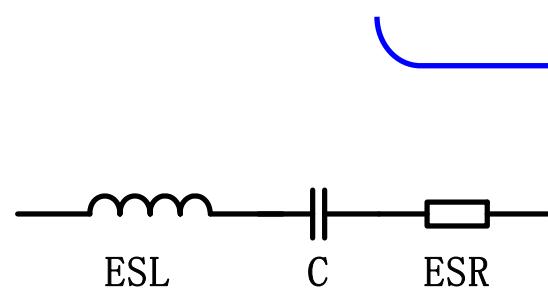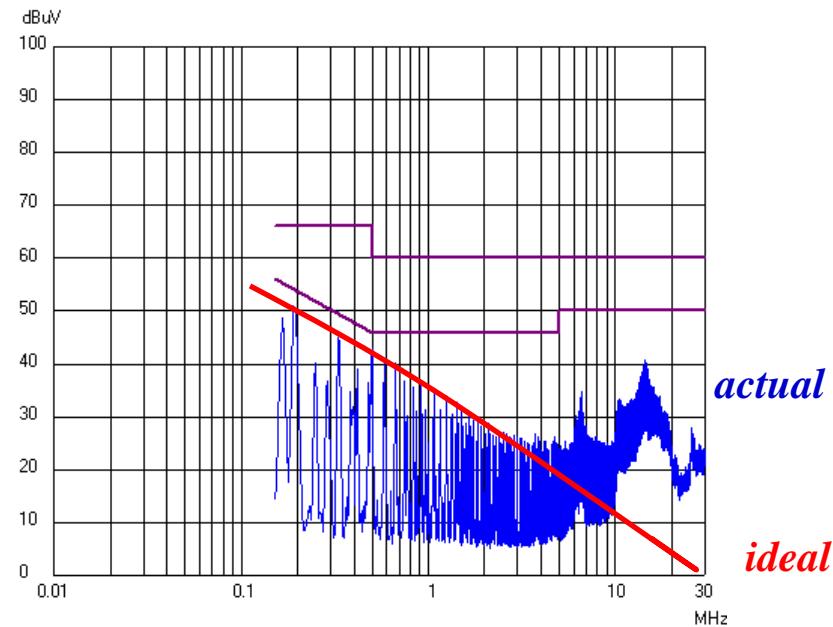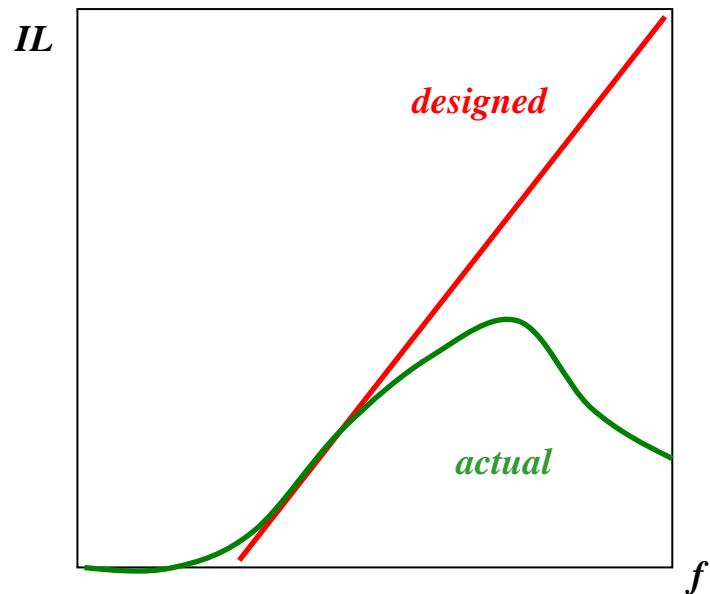

Capacitor Model

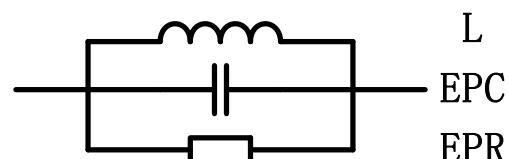


Inductor Model

## What to do?

Decrease parasitic as possible!

1: Using good HF capacitor or inductor! Small parasitic parameter!

对于电感:

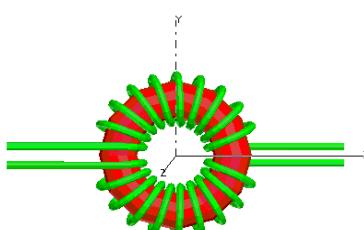

{ 铁氧体: 易饱和、导磁率高, 常用作共模扼流圈的磁芯  
锰锌:  $\mu_r = 500 \sim 10000$  for lower frequency CM choke  
镍锌:  $\mu_r = 10 \sim 100$  fit for HF CM choke

{ 采用少匝, 交错绕制等办法减小线圈的EPC!

# 非晶，纳米晶磁芯

特点：类似于锰锌铁氧体、高 $\mu$ , 高Bs, LF

用途：电感、变压器，LF CM choke

## 铁基非晶

饱和磁感应强度Bs	1.25 T	饱和磁致伸缩系数	$2 \times 10^{-6}$
居里温度Tc	560 °C	密度d	7.2 g/cm <sup>3</sup>
晶化温度Tx	510 °C	电阻率	130muOhm·cm
硬度Hv	880kg/mm <sup>2</sup>	热膨胀系数	

产品牌号	R-N-L	R-N-M
初始导磁率	$>3 \times 10^4$	$>8 \times 10^4$
最大导磁率	$>5 \times 10^4$	$>45 \times 10^4$

## 铁基纳米晶

饱和磁感应强度Bs	1.25 T	饱和磁致伸缩系数	$2 \times 10^{-6}$
居里温度Tc	560 °C	密度d	7.2 g/cm <sup>3</sup>

产品牌号	R-N-L	R-N-M	R-N-H
初始导磁率	$>3 \times 10^4$	$>8 \times 10^4$	$>1 \times 10^4$
最大导磁率	$>5 \times 10^4$	$>45 \times 10^4$	$>50 \times 10^4$

## 钴基非晶



产品牌号	R-N-L	R-N-M
初始导磁率	$>3 \times 10^4$	$>8 \times 10^4$
最大导磁率	$>5 \times 10^4$	$>45 \times 10^4$

饱和磁感应强度Bs	1.25 T	饱和磁致伸缩系数	$2 \times 10^{-6}$
居里温度Tc	560 °C	密度d	7.2 g/cm <sup>3</sup>
晶化温度Tx	510 °C	电阻率	130muOhm·cm
硬度Hv	880kg/mm <sup>2</sup>	热膨胀系数	


安泰

对于电容：


1：采用高频性能好的小电容。

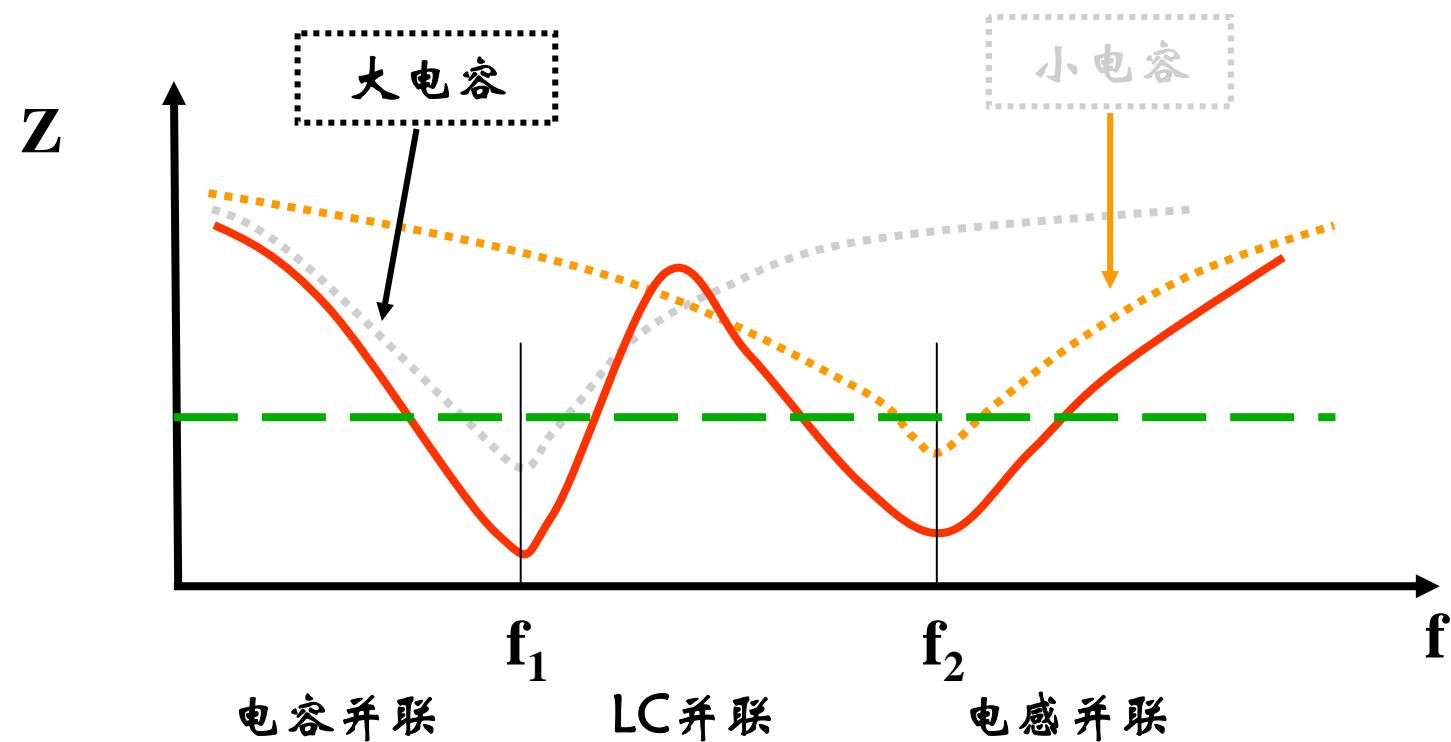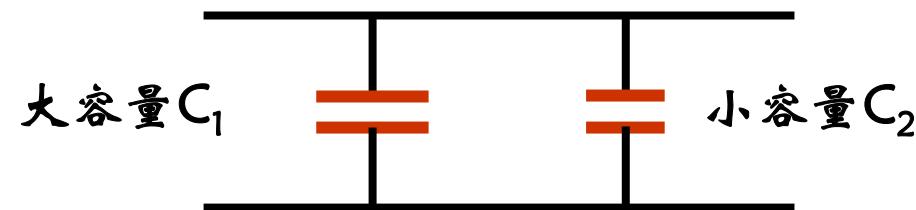




使用三端电容器

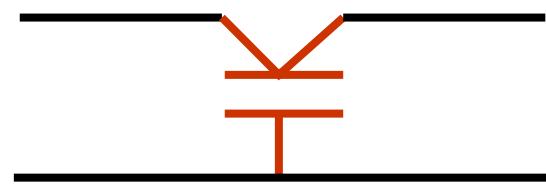

T型滤波电路


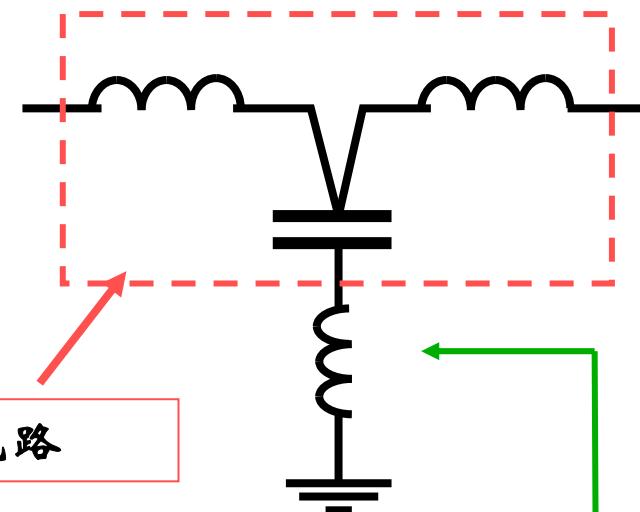


该引线电感有害，应尽量小  
该引线电感有害，应尽量小

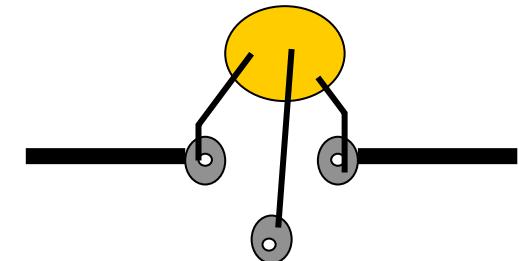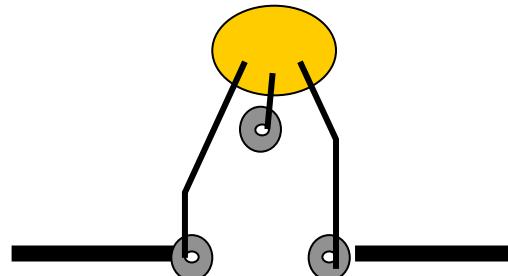
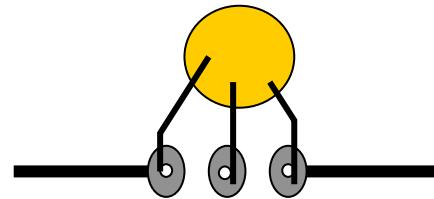


一些新型结构电容, x2y,

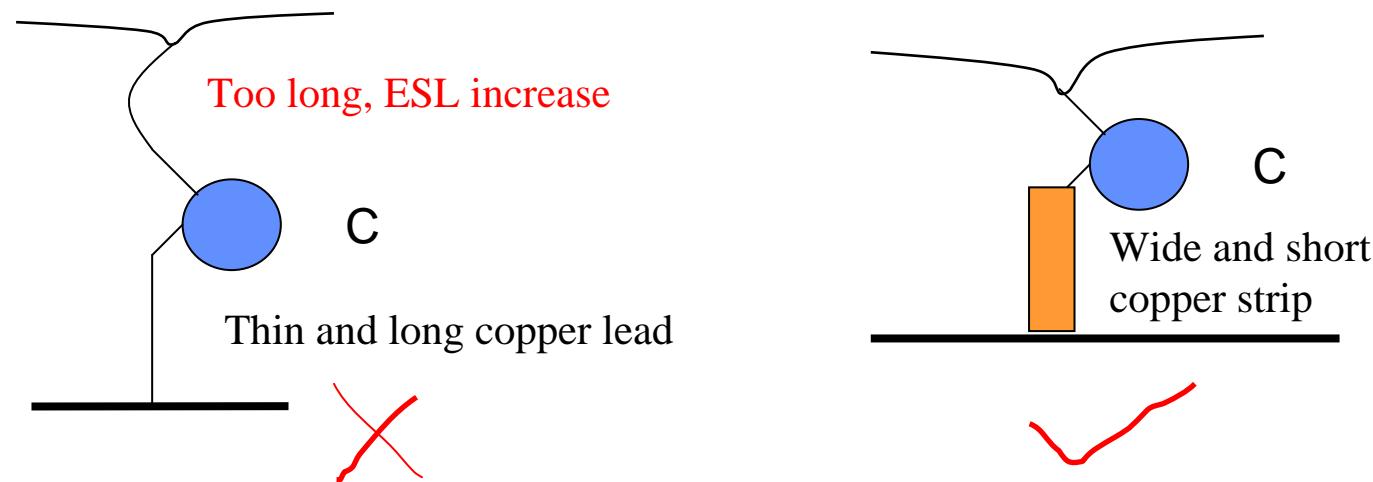
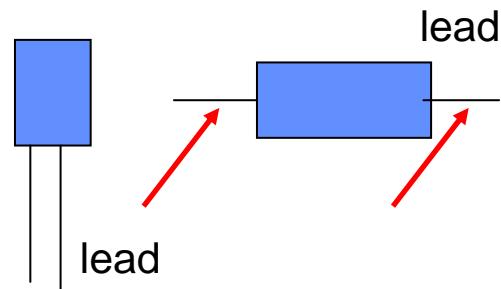
2: Decrease lead length of capacitor as shorter as possible. ESL!





### 3: Carefully installment!

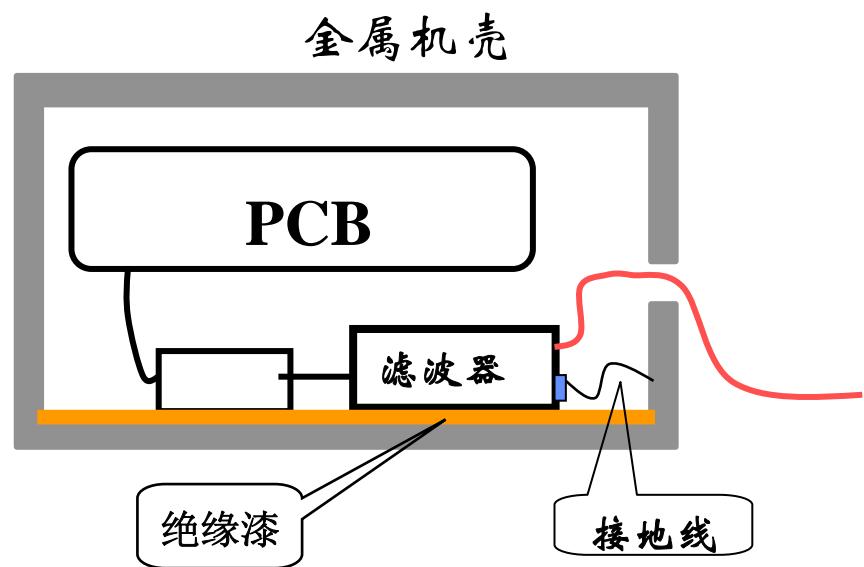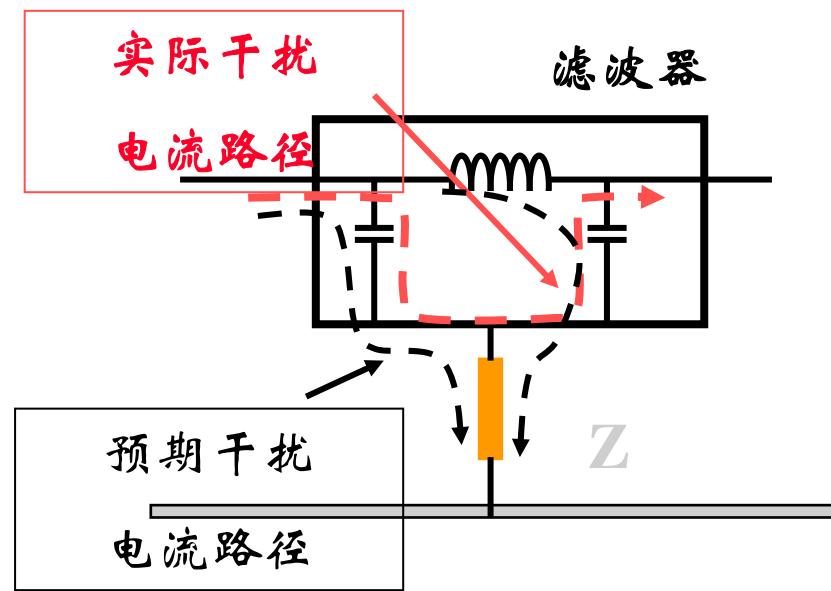

滤波器的输入输出引线应拉开距离，严禁并行走线和交叉走线。

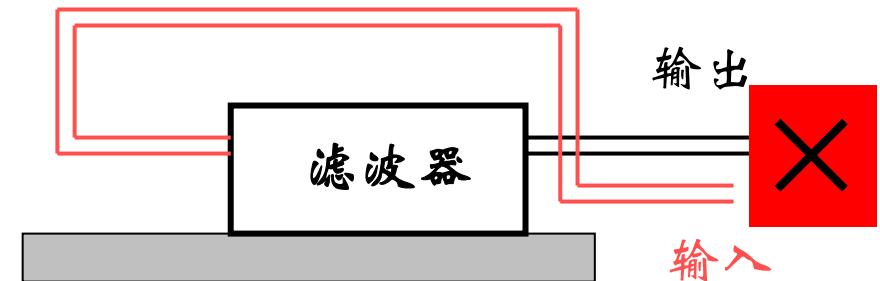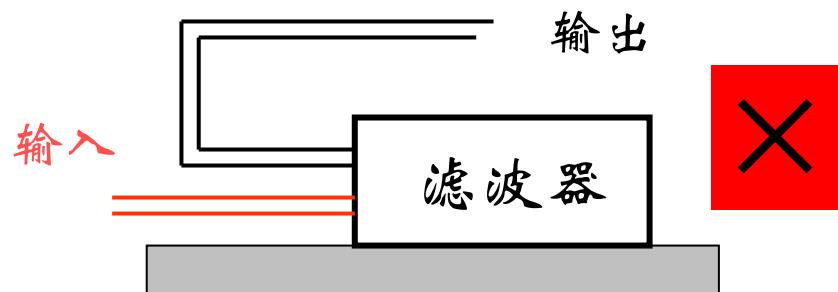

滤波器的输入、输出引线之间尽可能实现屏蔽隔离。

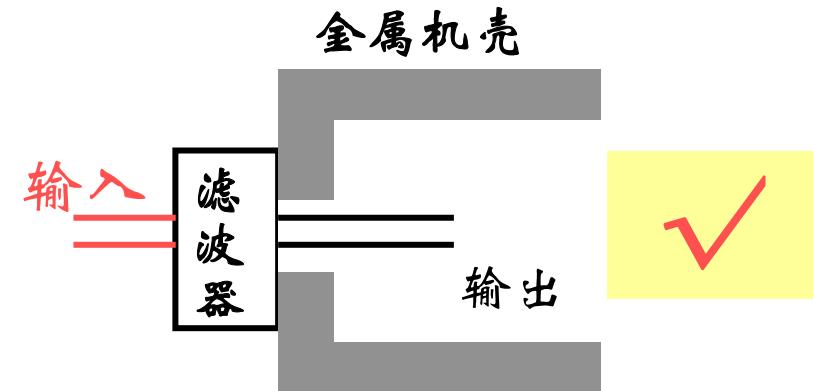
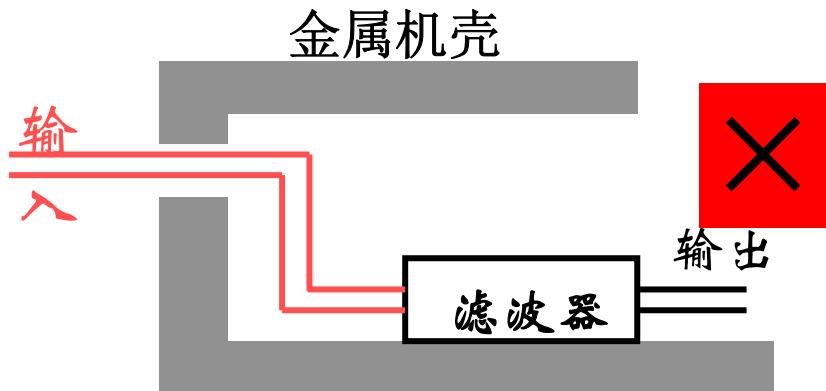



有源滤波器，可在 $150\text{kHz}$ -几 $\text{MHz}$ 有效




# Active EMI filter for DC/DC

## Picor Com

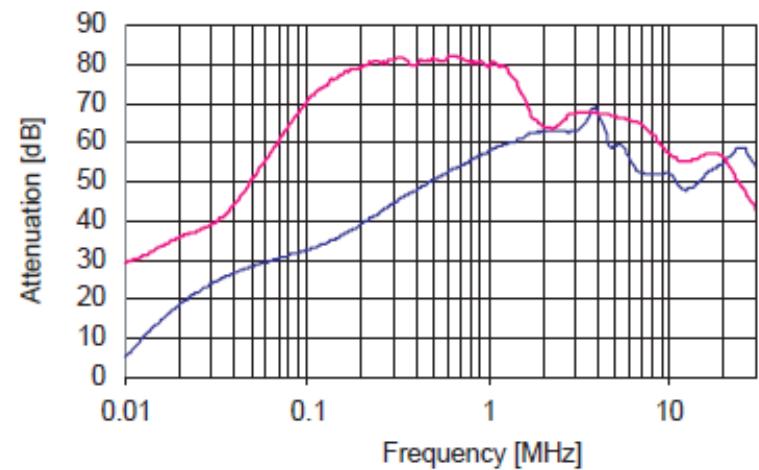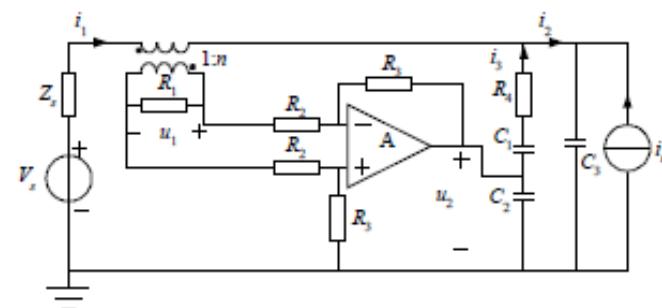


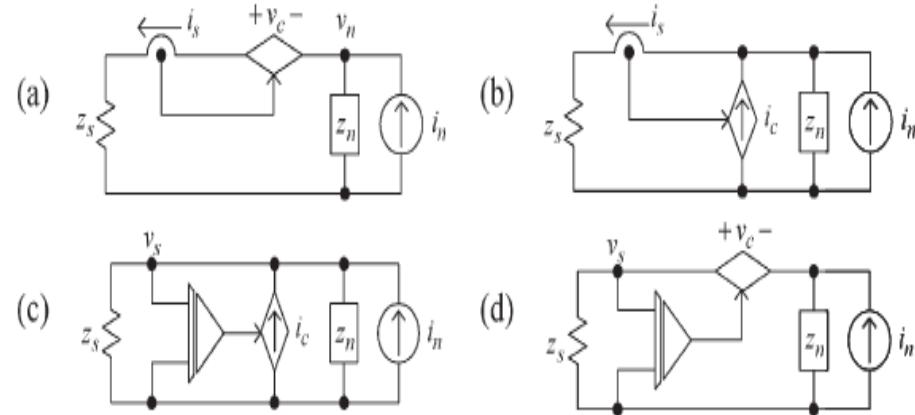

ALL active EMI filter topology

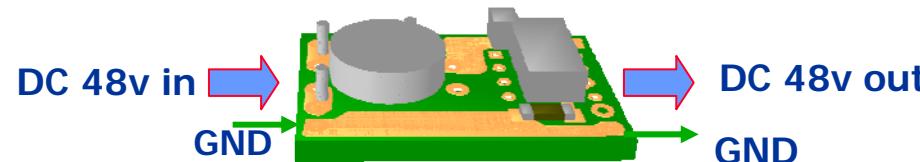


Delta/ Xjtu/

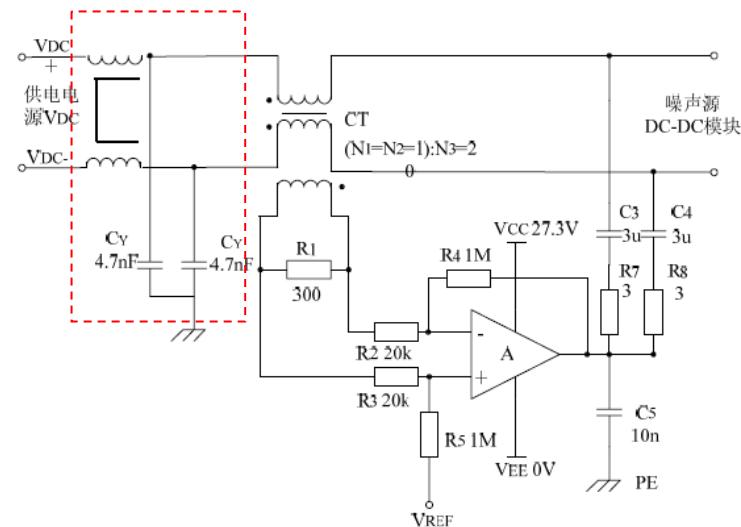

Hybird EMI filter





Emerison/ Hit

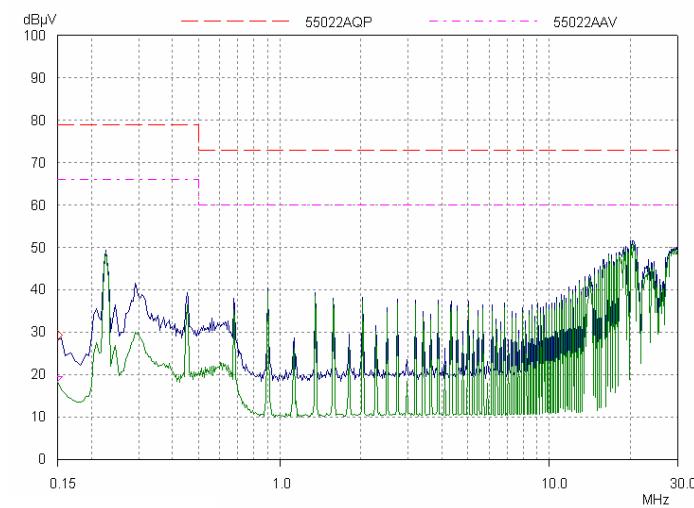

也用于逆变电源




Active Common Mode Noise  
Canceller

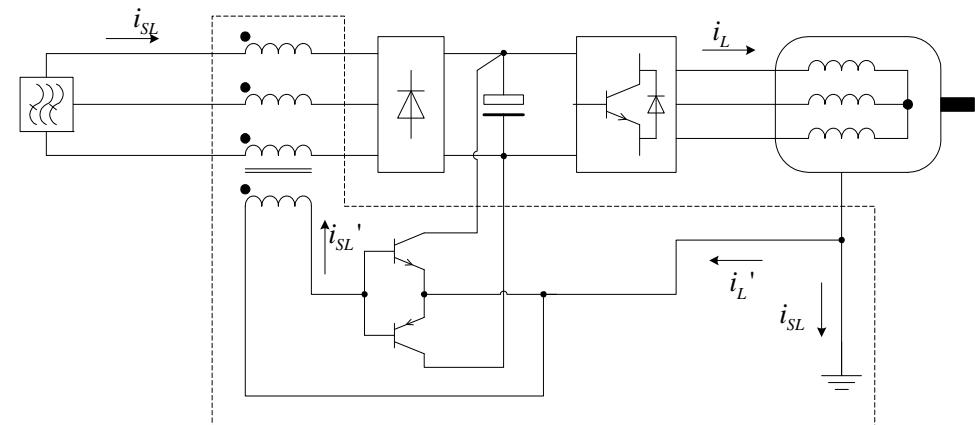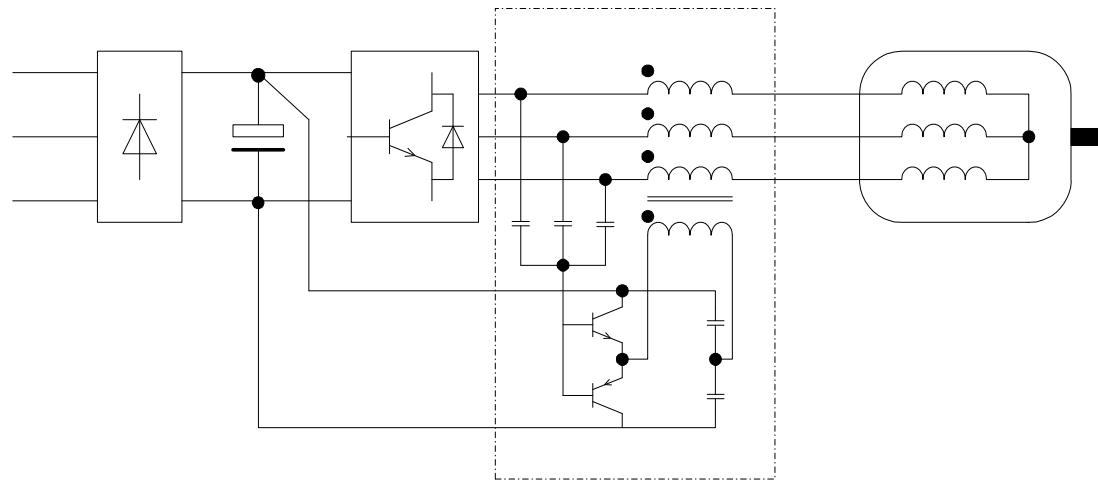

Active EMI Filter

三：根据电源拓扑、结构、控制等多种方面，采用新型抑制方法

### B1: 改善门极驱动

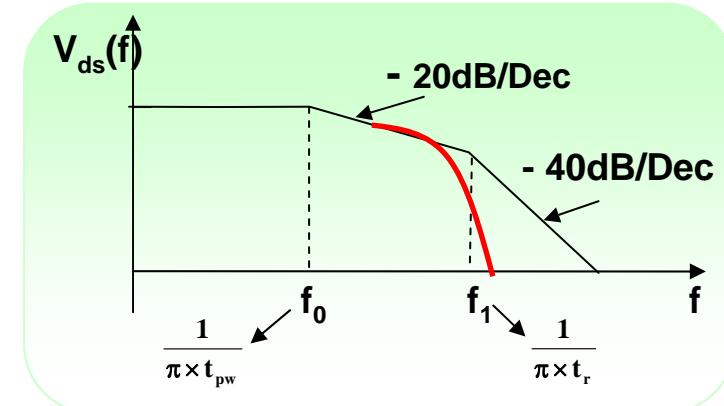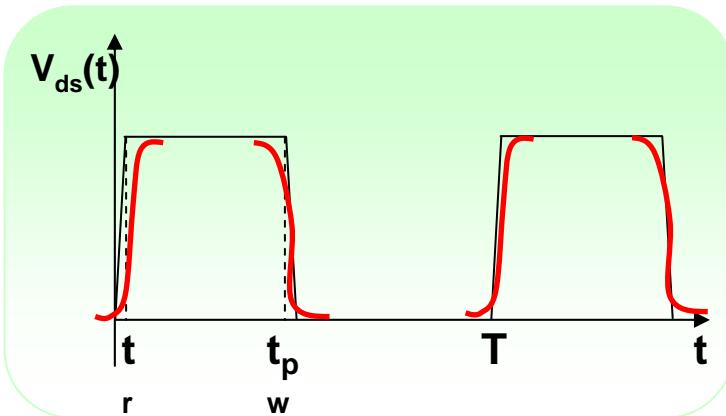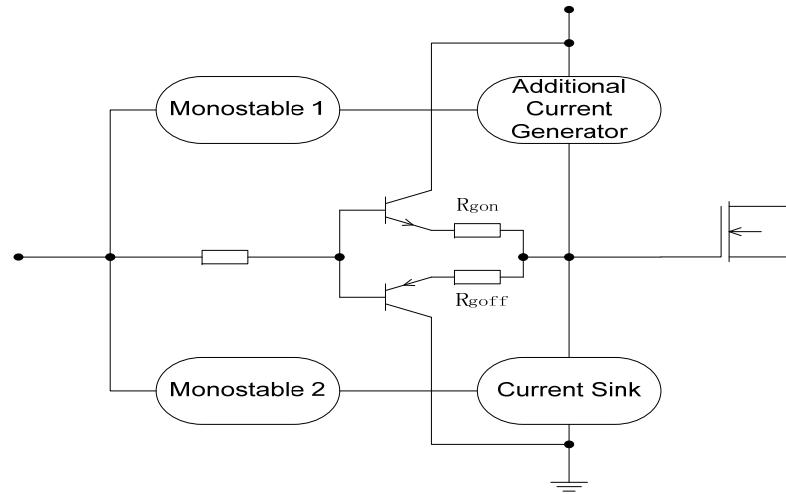


适当的驱动可使功率损耗和高频频谱得到平衡

已商业化。


## B2: 合适的软开关技术

City University of Hong Kong

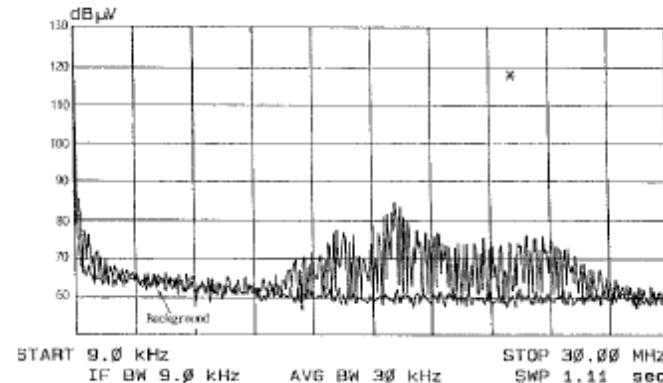

传导发射


## BUCK/BOOST/FLYBACK

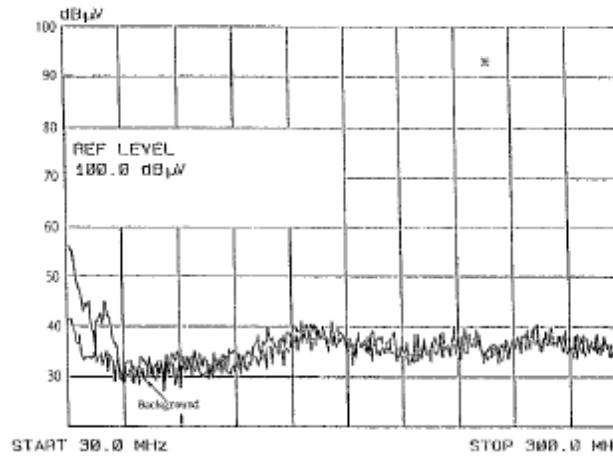


辐射发射

CPES

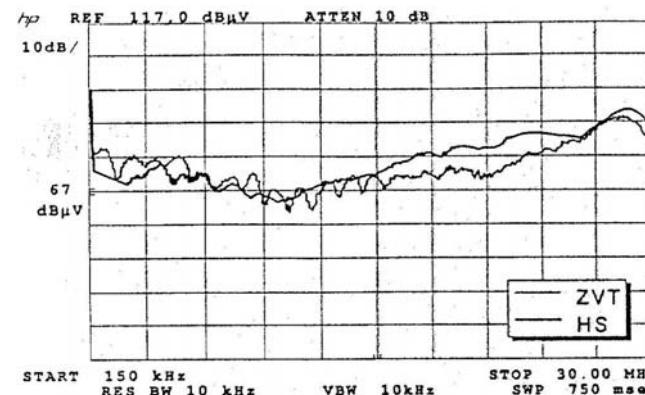Hard-switching vs. soft-switching of a inverter







L 线传导发射

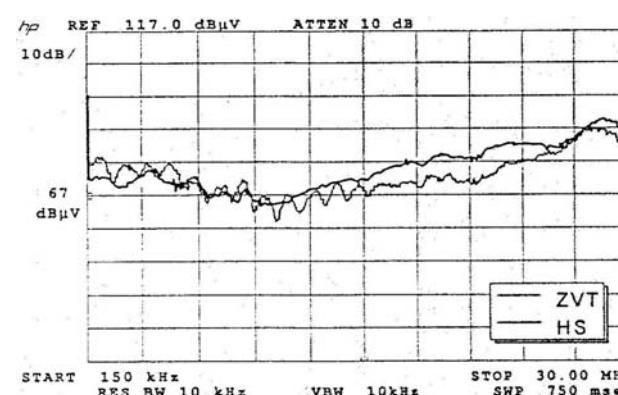

N 线传导发射


### B3: 反向补偿技术

Feedback Coil in the Boost Inductor

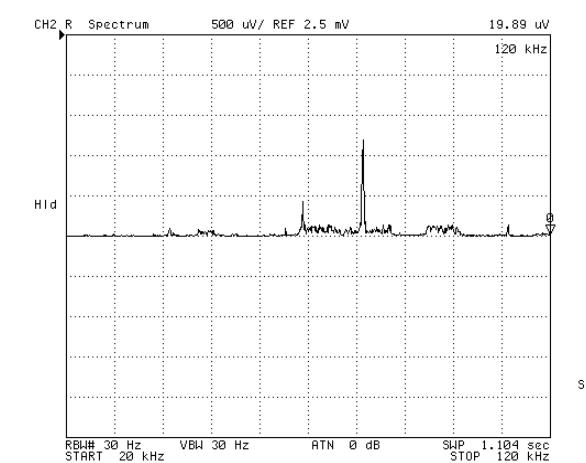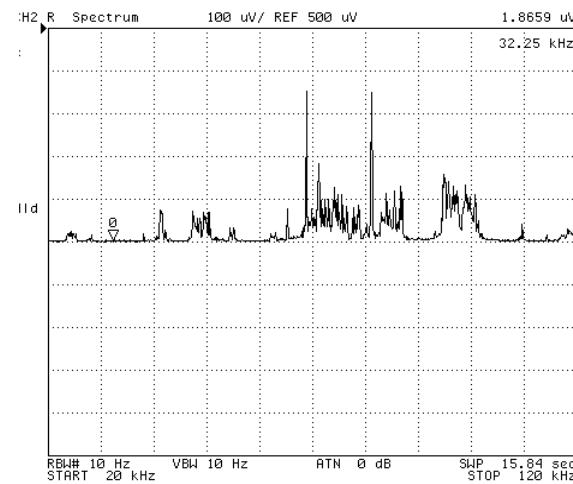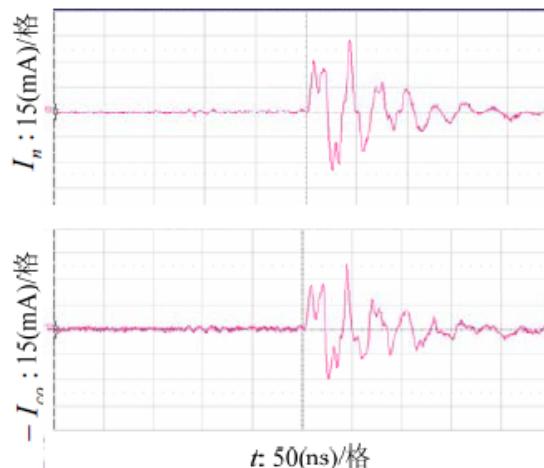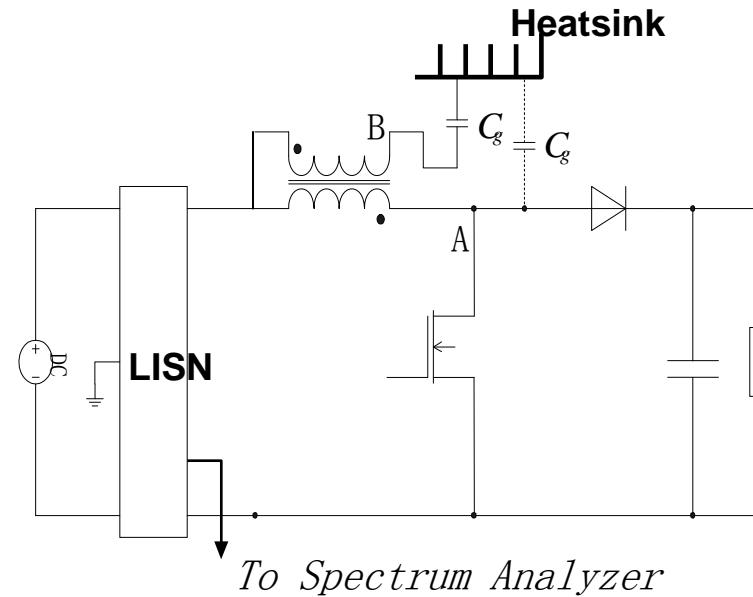



SELECT LETTER  
SPACE  
BACK SPACE  
ERASE TITLE  
DONE  
STOR DEV [DISK]  
CANCEL

## B4: 对称平衡结构→抑制共模发射的有效办法

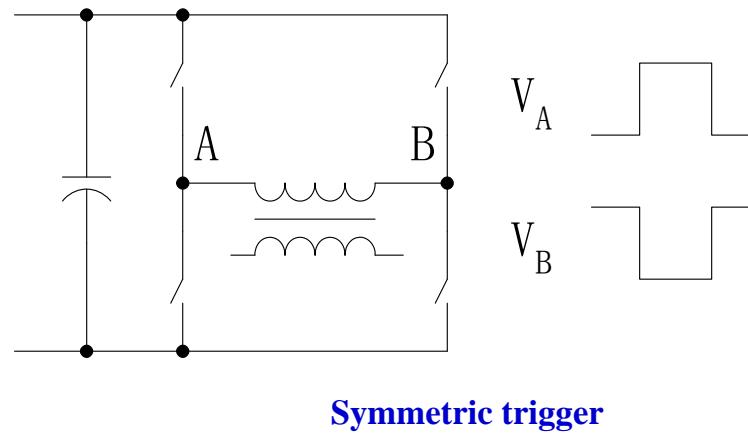




ZERO CM EMISSION!

FBSP bad CM emission!!

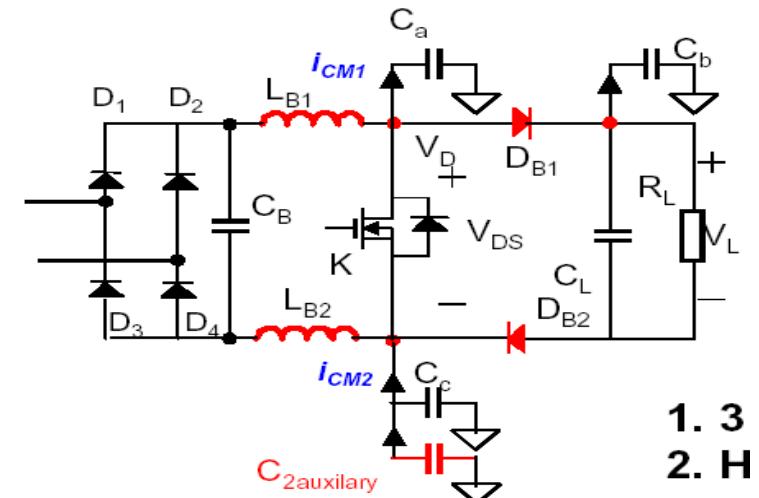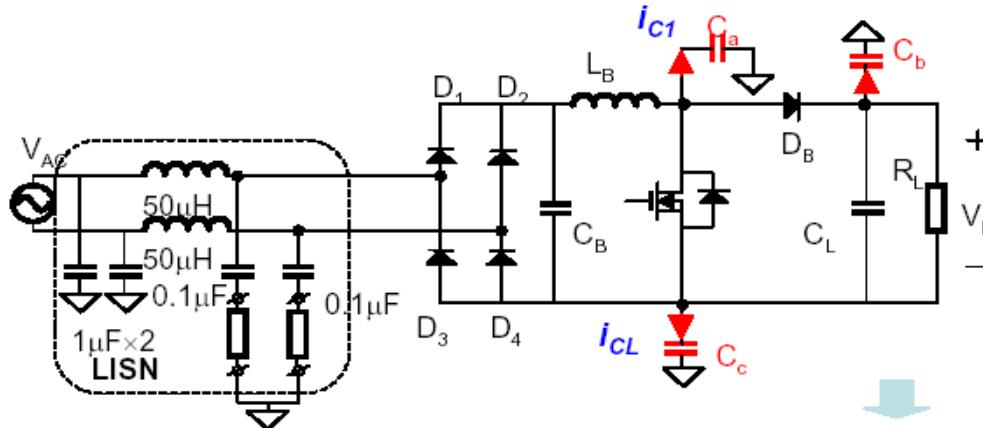



These principle has early been proposed in 90's and it can be used in any topology.  
Low effectiveness, high cost!

Dual Boost: CM Emission is large.

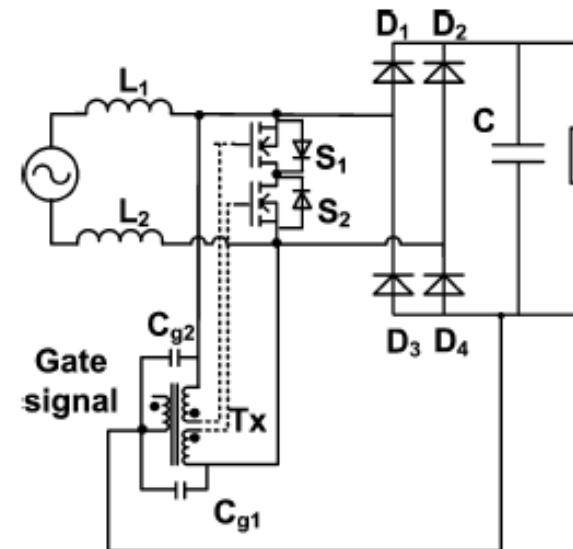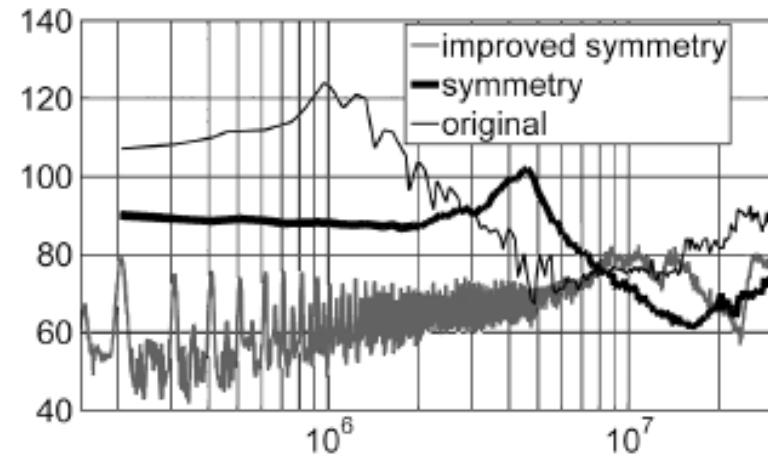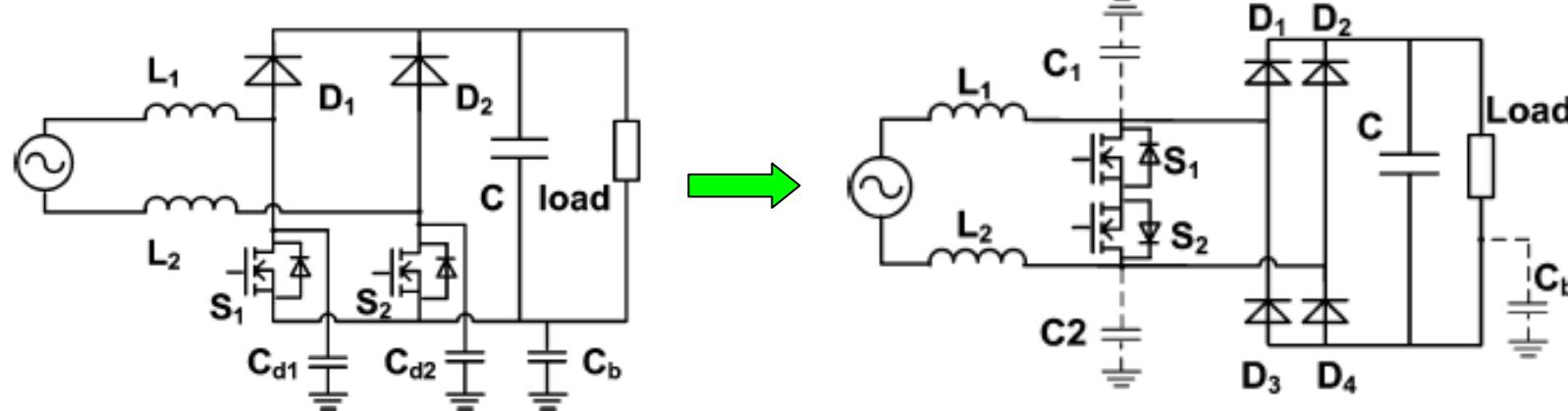


## B5: 巧用屏蔽

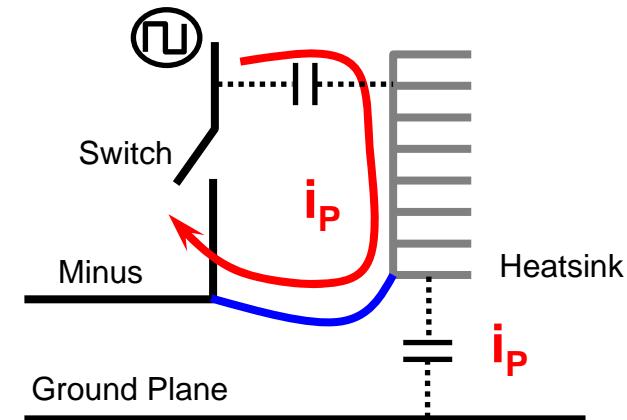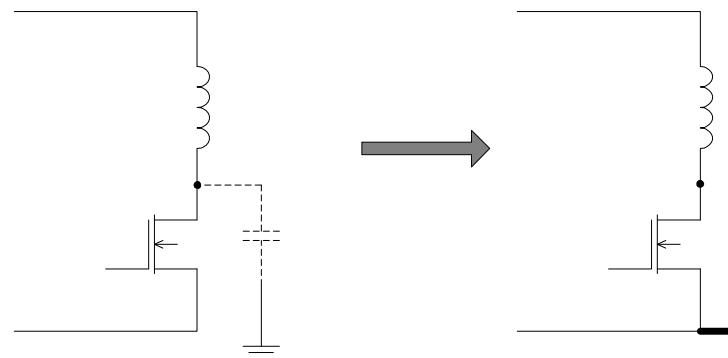
### 1. Heatsink Connected to the Minus bus



### 2 . Copper Foil around X'FORM

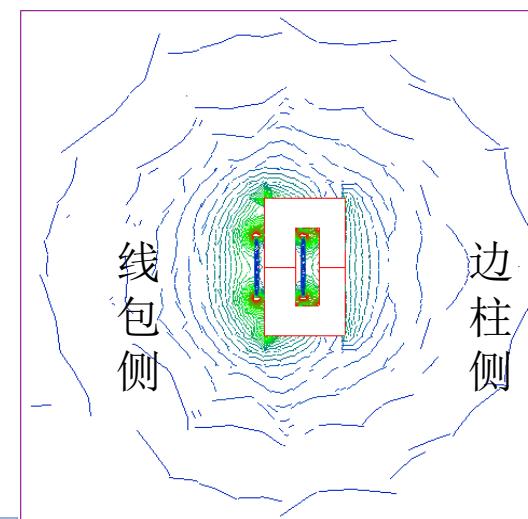
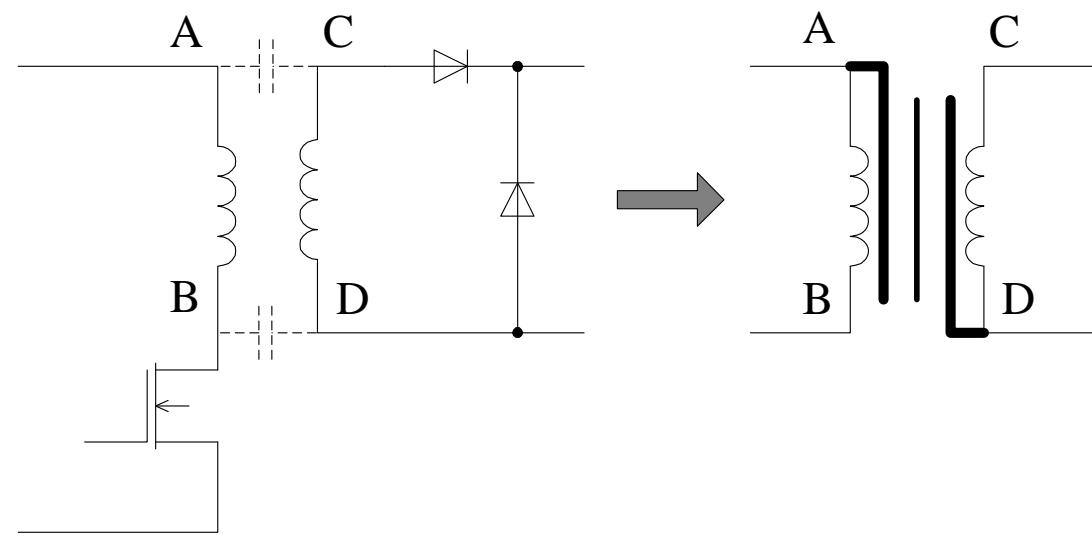
### 3: Shielding primary and secondary of transformer



*Delta com : USA patent 20070171585  
Method for suppressing common mode noise*

## B6: 频率调制技术

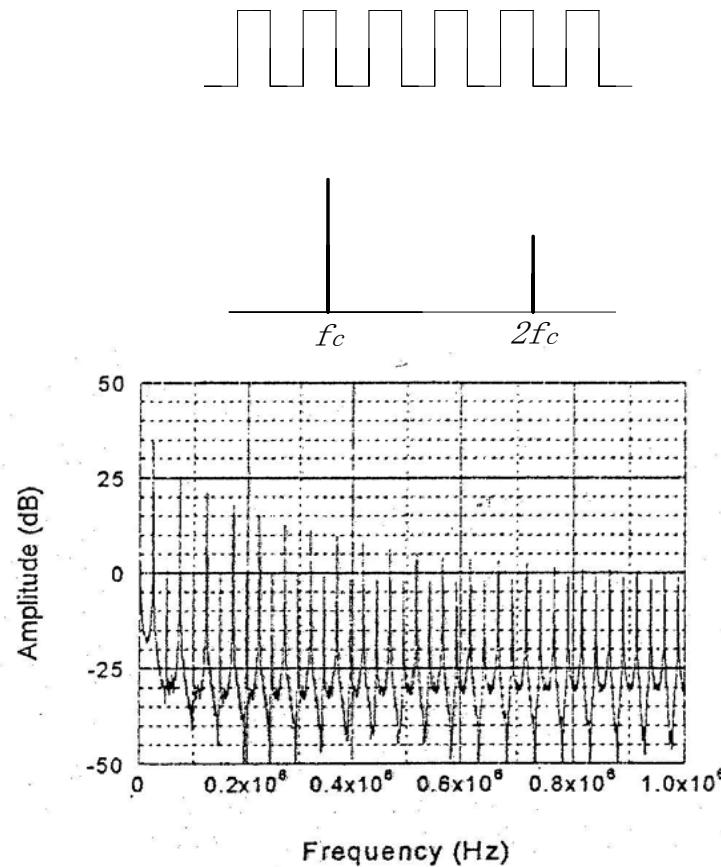


Fig 1a. Constant 25kHz PWM

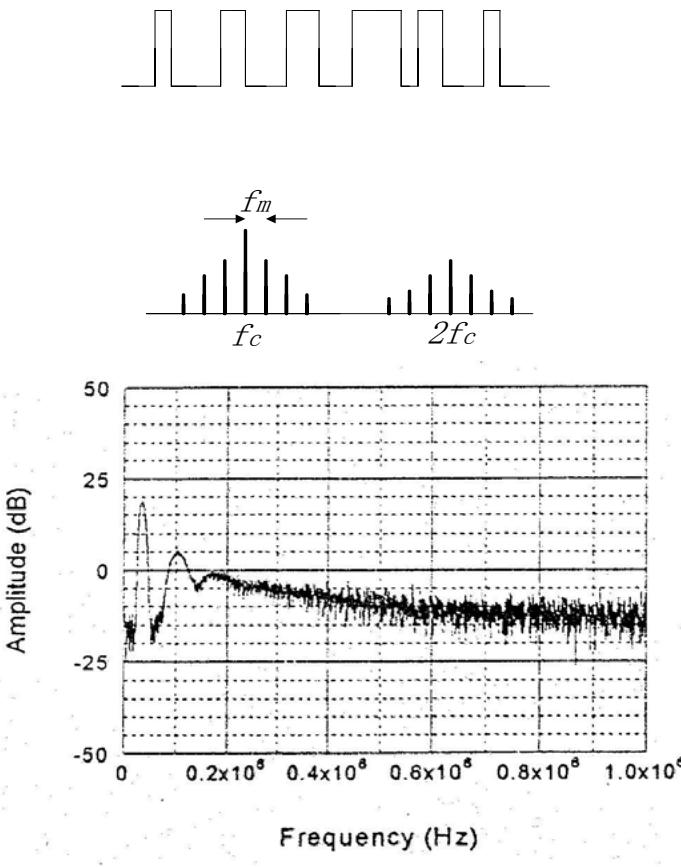


Fig 1c.  $\Delta f = 20\text{kHz}$  (frequency varied from 25kHz to 45kHz),  $n=256$ .

*Switching frequency modulation*  
— proposed by F. Lin et al , IEEE PESC'93



- **Random modulation**

\_\_\_\_\_ proposed by D.A. Stone et al, IEEE APEC'96

- **Sigma - Delta modulation**

\_\_\_\_\_ proposed by J. Paramesh et al, IEEE APEC'99



- **Comparison : PWM & RPWM [43]**

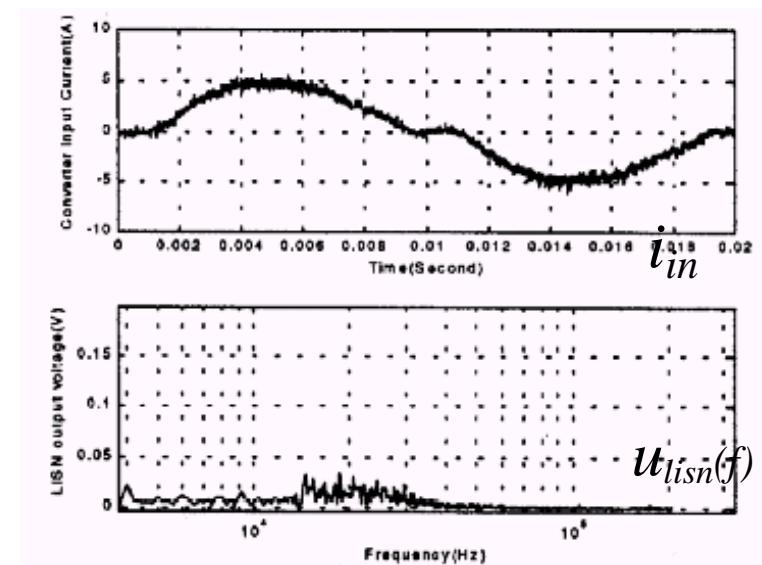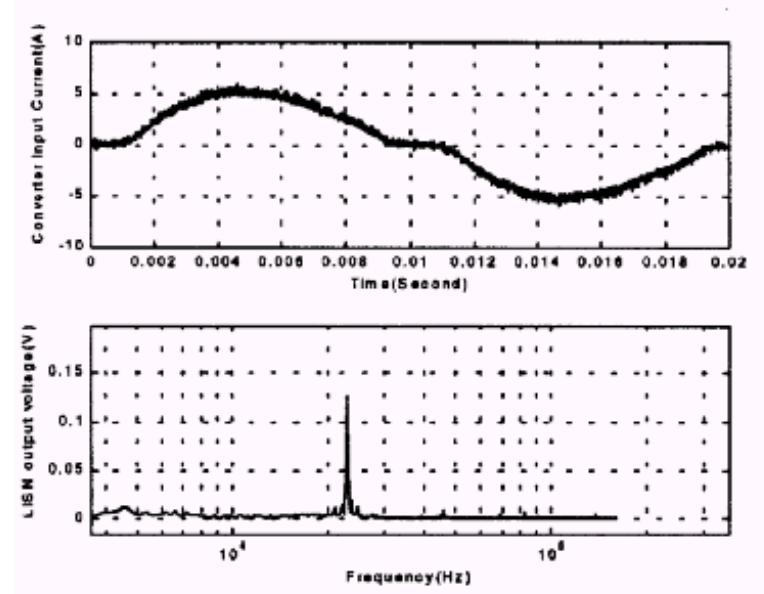

已商业化!



抖频幅度要大于10kHz. 输出直流有调制纹波!

## B7: 合理触发控制

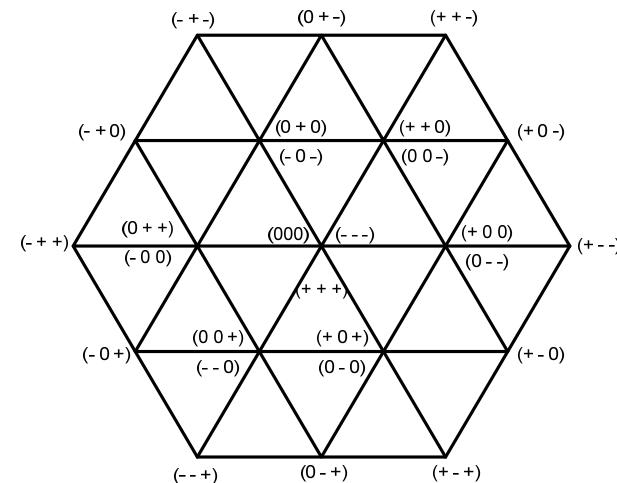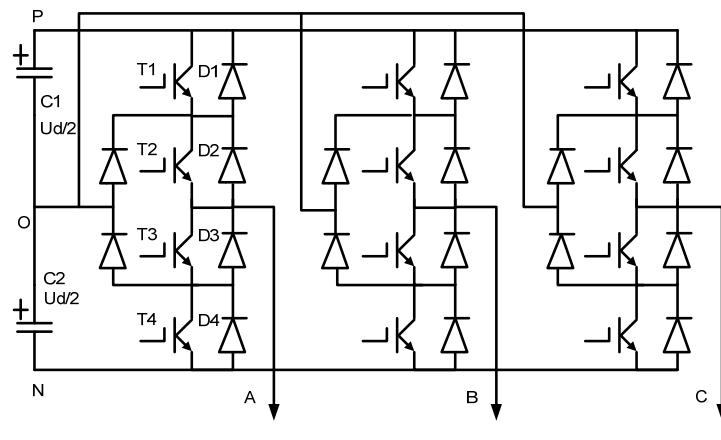

三电平逆变器共存在27状态， 存在 $U_a+U_b+U_c$ 小的SVPWM策略

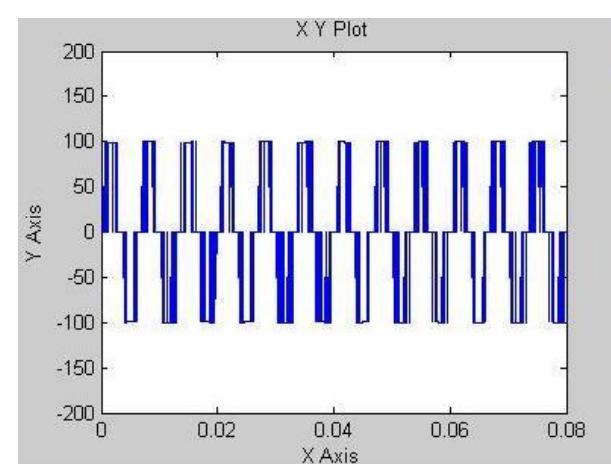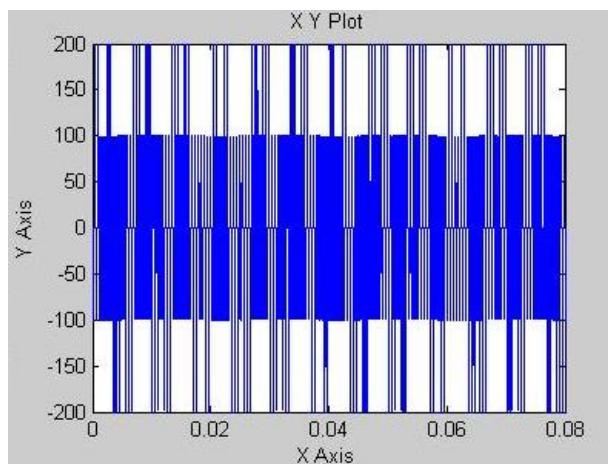CM Voltage 可从 $U_{bus}/3$ 降到 $U_{bus}/6$ ！




HIT for SIEMENS

## B8: PCB精心设计

减小 $dv/dt$ 导体面积，减小 $di/dt$ 回路面积！  
敏感电路远离高 $dv/dt$ 、 $di/dt$ 点！


### MAXWELL Software Assistant Method

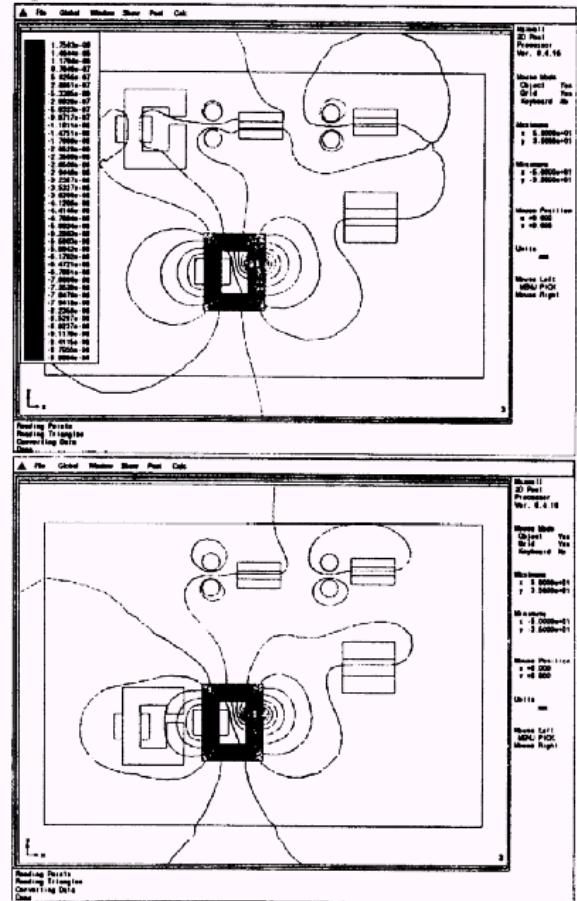

(a) Flux plot of quasi-resonant boost converter with basic layout

(b) Flux plot of quasi-resonant converter with changed good layout





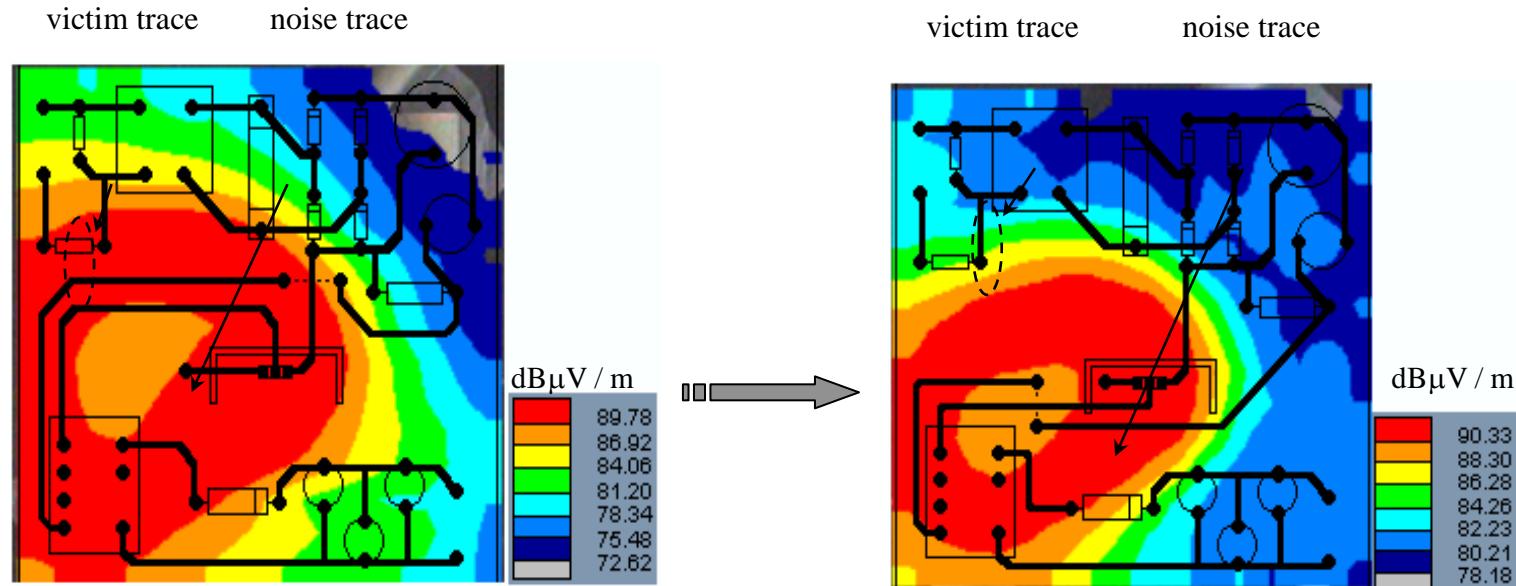
## Routing Traces by Electrical Field Emission scan




— proposed by X. Wu Zhejiang Univ, IEEE APEC'99



- The victim trace in weaker emission area is likely to pick up less noise;
- PCB designers can arrange critical trace in suitable position to receive less interference according to emission map.

## 四：EMI滤波器的特殊问题

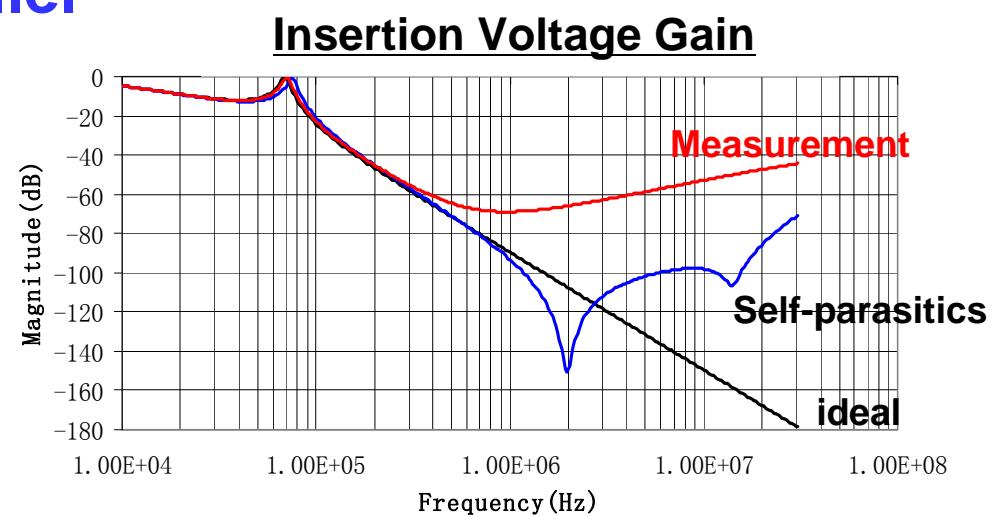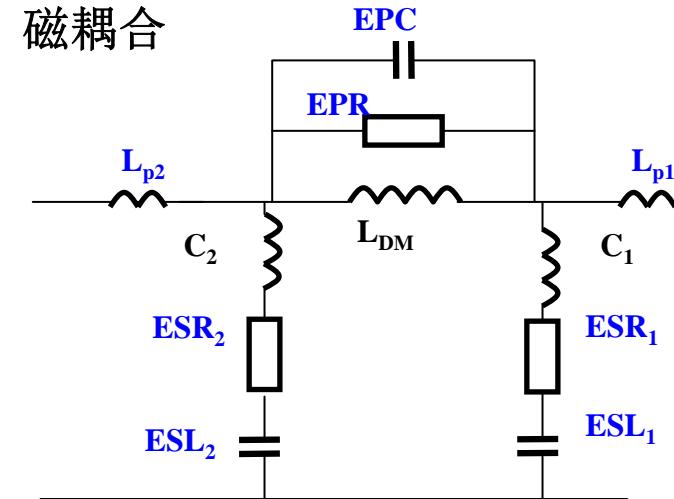
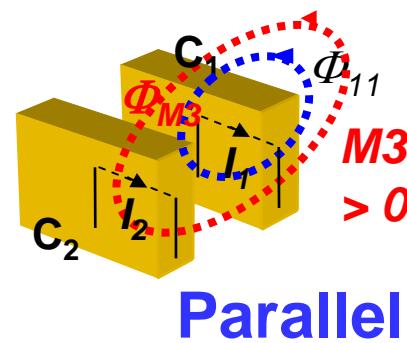
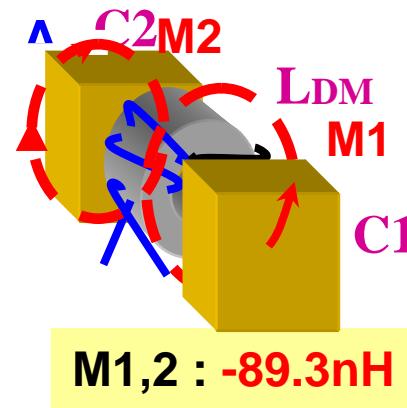
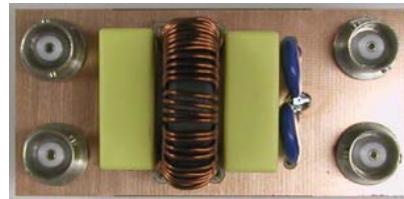


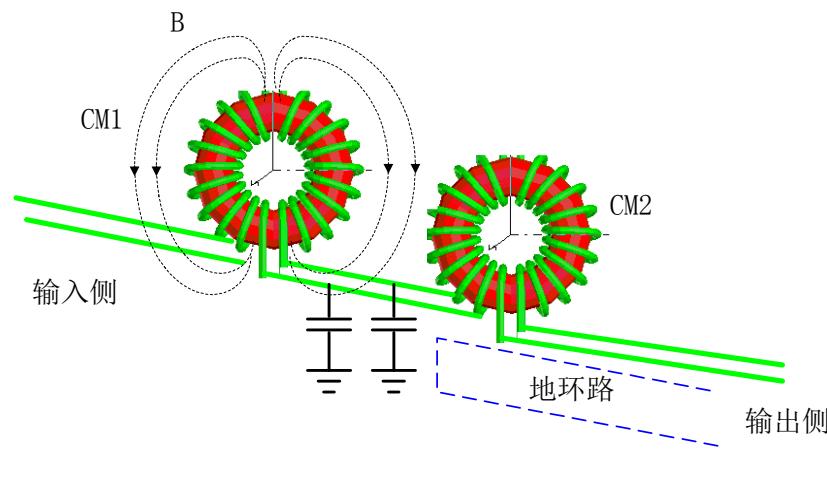


## 电耦合

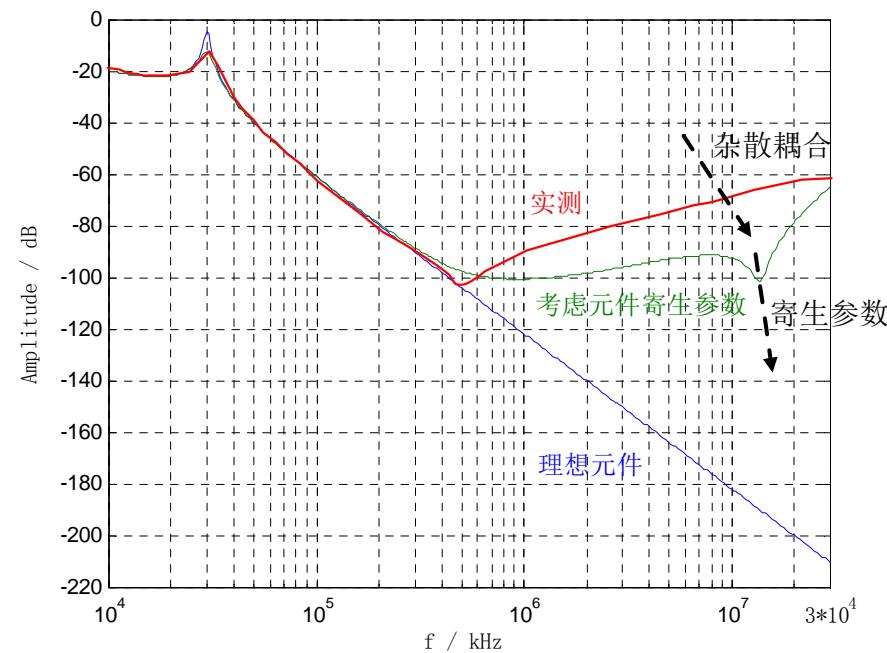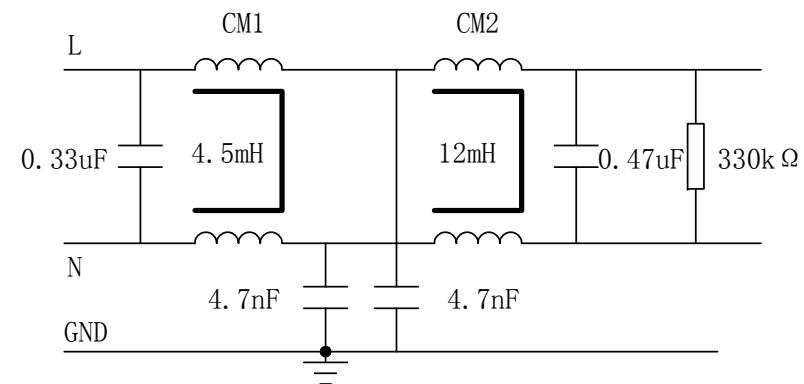


## 寄生参数/耦合的抑制

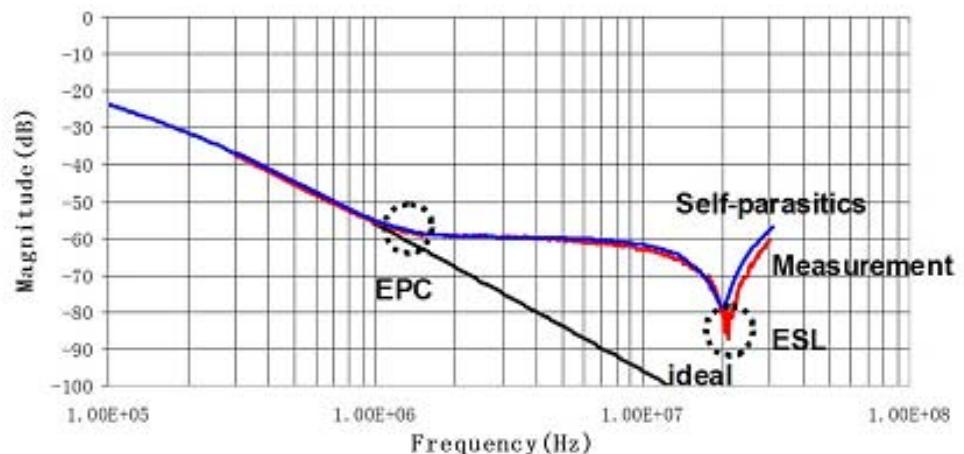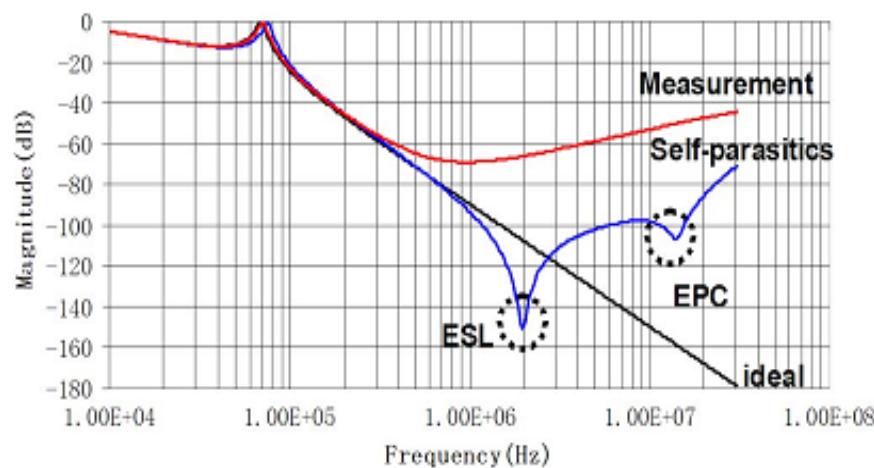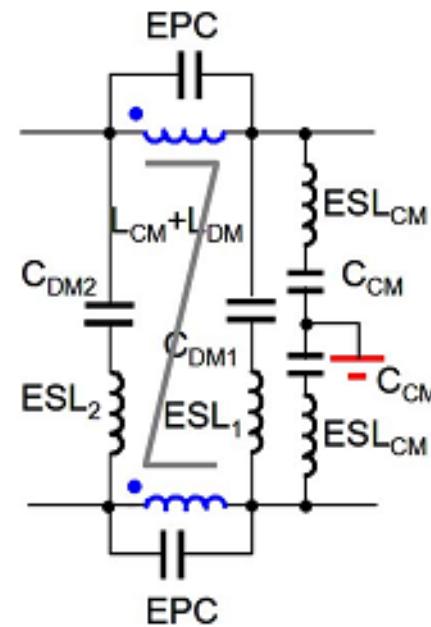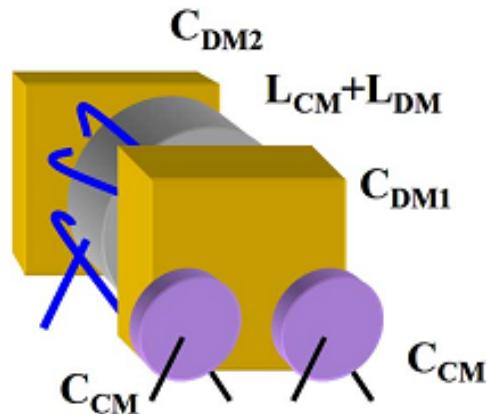


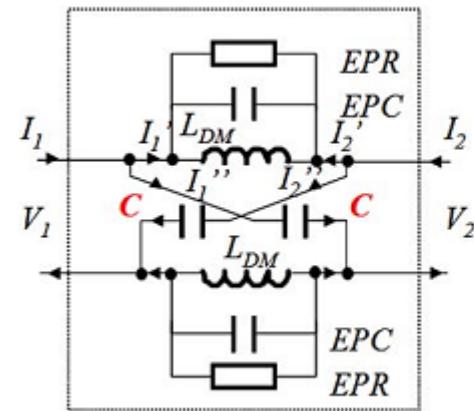


**C=EPC**

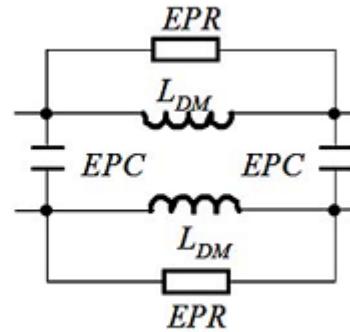


**No EPC**

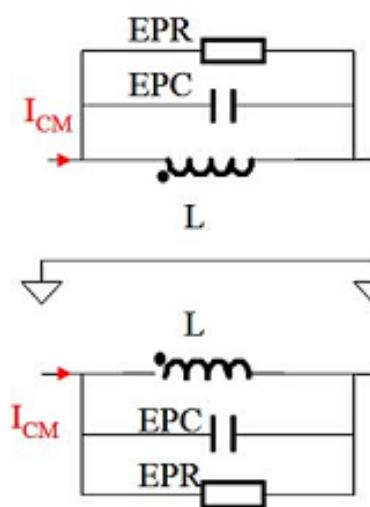

**K=1**

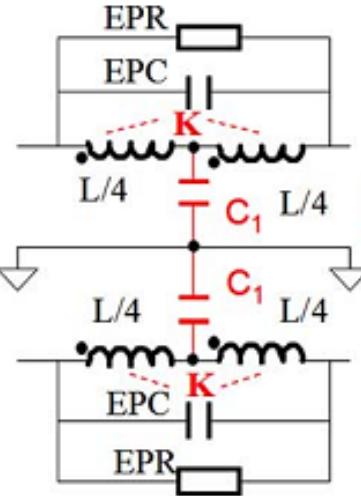

If  $C_1 = 4EPC$

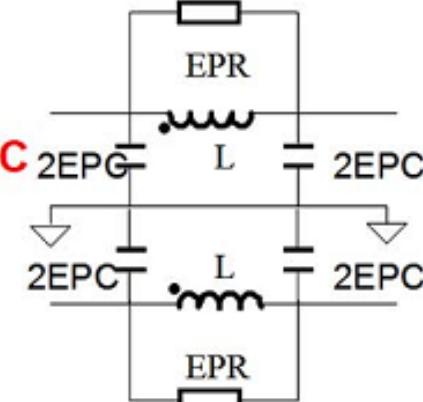


**NO EPC**





(a)

(b)







(c)

电感EPC的抑制

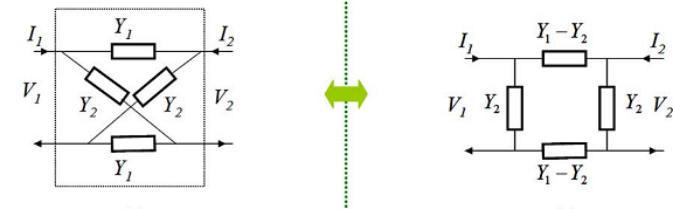

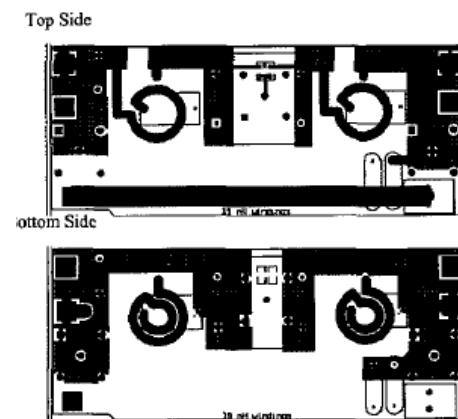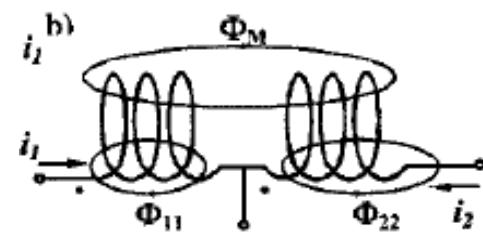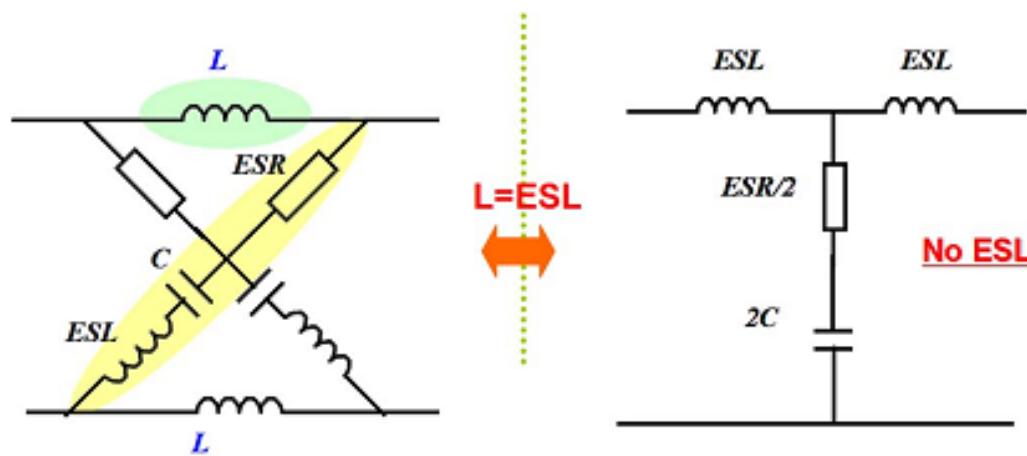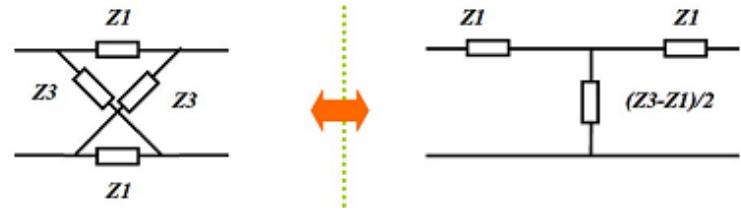


电容ESL抑制

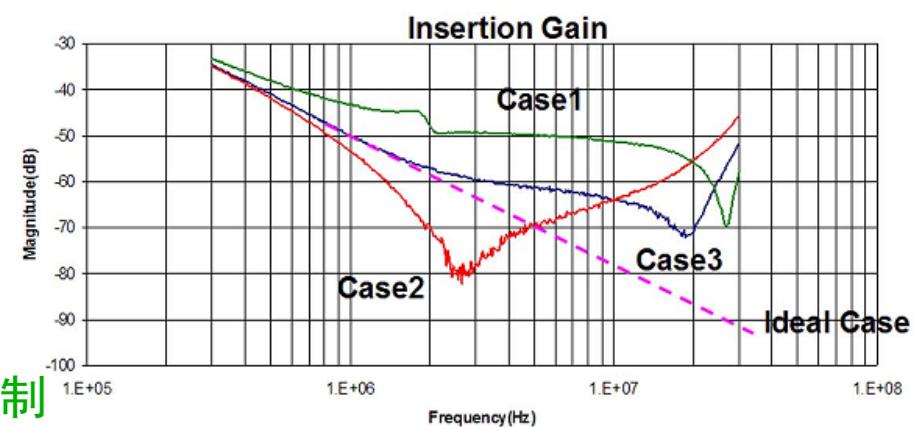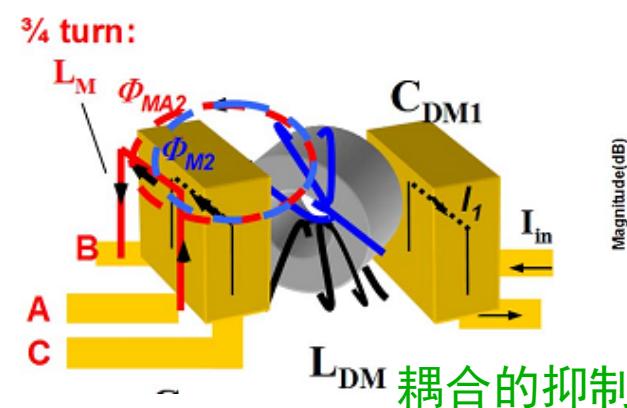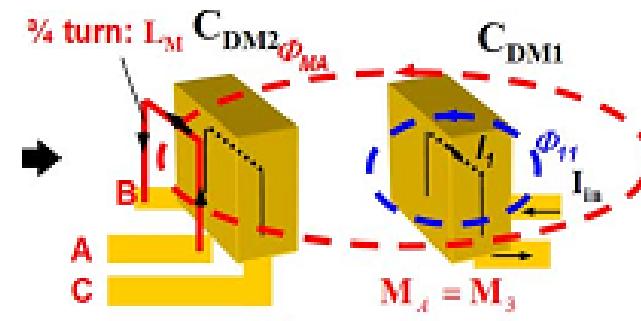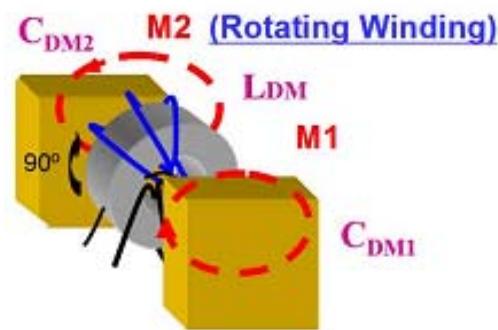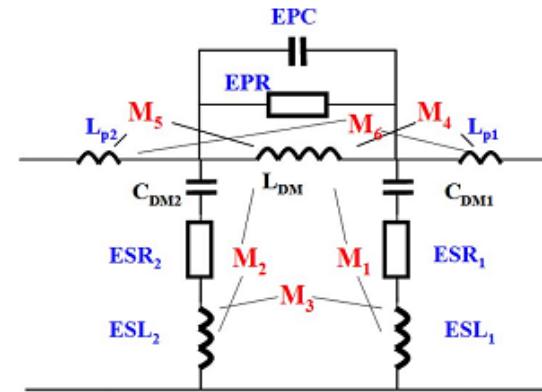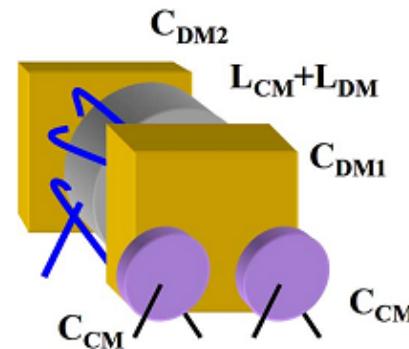

*Any questions?*



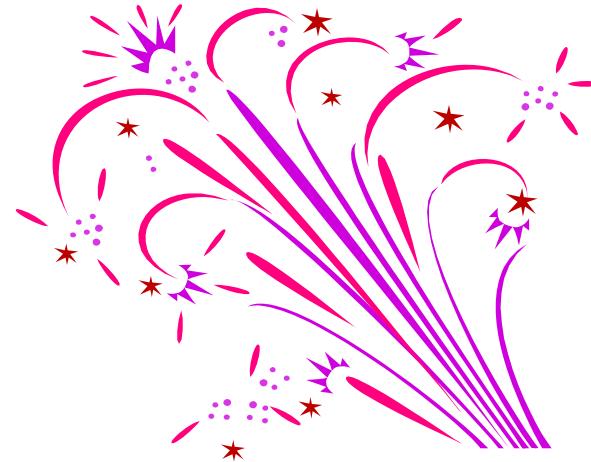

*Thanks for your attention!*

谢谢大家！